

# MIPS design

Isaac Pérez Andrade

ITESM Guadalajara  
Department of Engineering & Architecture  
Department of Computer Science

August - December 2020



# A basic Microprocessor

# Basic $\mu$ P

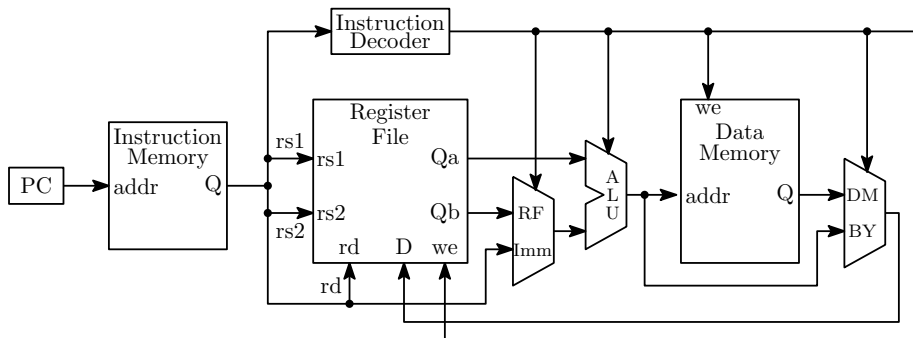


Figure 1: Generalised Microprocessor ( $\mu$ P) schematic.

# Basic $\mu$ P

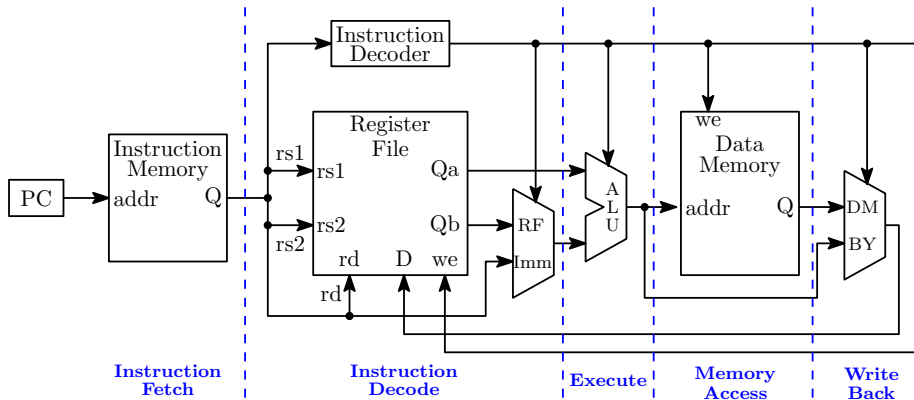


Figure 2: Stages of a  $\mu$ P cycle.

# Stages of a basic $\mu$ P instruction cycle

1. **Instruction Fetch (IF)**. Instructions are read from Instruction Memory (IM).
2. **Instruction Decode (ID)**. Type of operation and operands are defined.
3. **Execute (EXE)**. Operands are used in order to perform arithmetic or logical operations.
4. **Memory Access (MEM)**. Data is read/written from/to Data Memory (DM).
5. **Write Back (WB)**. Results from EXE or MEM stages are written back into Register File (RF).

# MIPS example

- Microprocessor without Interlocked Pipeline Stage (MIPS) is a Reduced Instruction Set Computer (RISC)-type  $\mu$ P.
- MIPS flavours could use 16, 32- or 64-bits data widths.
- Supports 3 main instruction types.
  - R-Type for register-register operations.
  - I-Type for immediate operations.
  - J-Type for jump operations.

# MIPS instruction encoding

 


Figure 3: Example of MIPS encoding.

- **op**: Basic operation of the instruction, traditionally called **opcode**.
- **rs**: First register source operand.
- **rt**: Second register source operand.
- **rd**: Destination register.
- **sa**: Shift amount.
- **func**: Function. Specifies a variant of the operation in the op field.



# MIPS instruction encoding

- Considering the previous encoding
  - What type(s) of addressing modes are available?
  - How many registers can we access?
  - Can we access data from the memory?
- Since MIPS is a RISC, we can't simply add bits to the encoding.
  - Why?
- Instead, we must use the same 32-bits for accessing memory.
- For this purpose, some of the fields will have to be modified.

# MIPS instruction encoding

 


Figure 4: Example of another MIPS encoding.

- This format will allow us to access memory using a 16-bit address.
- This will also allow us to use immediate values (constants) for arithmetic and logical operations.

# MIPS instruction encoding

These are the encodings for each of the 3 main MIPS instruction types.

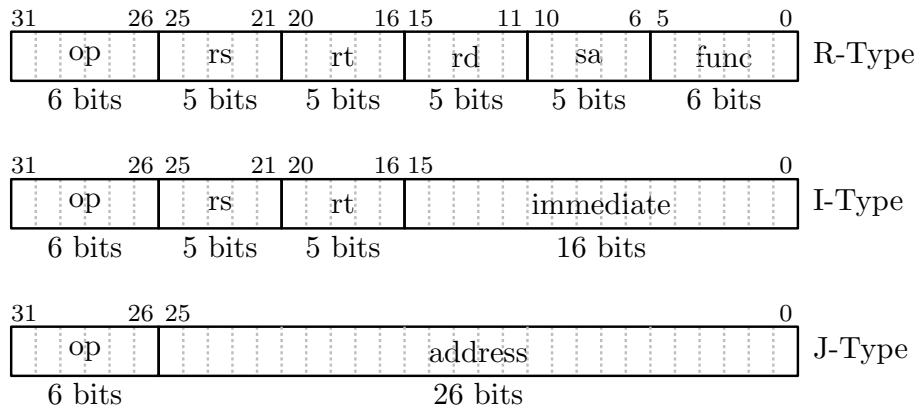


Figure 5: MIPS32 instruction types.

# MIPS instruction fields

- **op:** Basic operation of the instruction, traditionally called **opcode**.
- **rs:** First register source operand.
- **rt:** Second register source operand.
- **rd:** Destination register.
- **sa:** Shift amount.
- **func:** Function. Specifies a variant of the operation in the op field.
- **immediate:** A value that defines an address or a constant.
- **address:** An absolute address value.

Inst.	[31:26]	[25:21]	[20:16]	[15:11]	[10:6]	[5:0]	Meaning
add	000000	rs	rt	rd	00000	100000	Register add
sub	000000	rs	rt	rd	00000	100010	Register subtract
and	000000	rs	rt	rd	00000	100100	Register AND
or	000000	rs	rt	rd	00000	100101	Register OR
xor	000000	rs	rt	rd	00000	100110	Register XOR
sll	000000	00000	rt	rd	sa	000000	Shift left
srl	000000	00000	rt	rd	sa	000010	Logical shift right
sra	000000	00000	rt	rd	sa	000011	Arithmetic shift right
jr	000000	rs	00000	00000	00000	001000	Register jump
addi	001000	rs	rt		Immediate		Immediate add
andi	001100	rs	rt		Immediate		Immediate AND
ori	001101	rs	rt		Immediate		Immediate OR
xori	001110	rs	rt		Immediate		Immediate XOR
lw	100011	rs	rt		offset		Load memory word
sw	101011	rs	rt		offset		Store memory word
beq	000100	rs	rt		offset		Branch on equal
bne	000101	rs	rt		offset		Branch on not equal
lui	001111	00000	rt		immediate		Load upper immediate
j	000010			address			Jump
jal	000011			address			Call

Figure 6: MIPS32 integer instructions.

# MIPS instruction examples

Table 1: MIPS instruction examples

Instruction	Meaning
add rd, rs, rt	$rd \leftarrow rs + rt$
addi rt, rs, imm	$rt \leftarrow rs + (\text{sign\_ext})imm$
ori rt, rs, imm	$rt \leftarrow rs \mid (\text{zero\_ext})imm$
sra rd, rt, sa	$rd \leftarrow rt \ll sa$
lui rt, imm	$rt \leftarrow imm \ll 16$
lw rt, offset(rs)	$rt \leftarrow \text{memory}[rs + \text{offset}]$
sw rt, offset(rs)	$\text{memory}[rs + \text{offset}] \leftarrow rt$
bne rs, rt, label	if $(rs \neq rt)$ then $PC \leftarrow \text{label}$
j target	$PC \leftarrow \text{target}$
jr rs	$PC \leftarrow rs$

# MIPS encoding example

Use [MIPS encoding format](#) in order to translate the following assembler code to machine code.

1. `add r4, r5, r6`
2. `sub r4, r5, r6`
3. `subu r4, r5, r6`
4. `addi r7, r8, -10`
5. `addiu r7, r8, -2`
6. `and r7, r8, r6`
7. `andi r7, r8, -1`
8. `lw r12, 100(r4)`
9. `sw r12, 100(r4)`
10. `lw r12, -100(r4)`
11. `sw r12, -100(r4)`
12. `j 1234`
13. `jr r23`

# MIPS encoding example

add r4, r5, r6

Mnemonic	add
Description	Adds two registers and stores result in a register.
Operation	$rd = rs + rt$
Syntax	add <i>rd</i> , <i>rs</i> , <i>rt</i>
Encoding	0000 00 <i>ss</i> <i>sss</i> <i>t</i> <i>tttt</i> <i>dddd</i> <i>d</i> 000 00 10 0000

- add r4, r5, r6 is encoded as

0000 00 00 101 0 0110 0010 0 000 00 10 0000  
00A62020



# MIPS encoding example

sub r4, r5, r6

Mnemonic	sub
Description	Subtracts two registers and stores result in a register.
Operation	$rd = rs - rt$
Syntax	sub rd, rs, rt
Encoding	0000 00 ss sss t tttt dddd d 000 00 10 0010

- sub r4, r5, r6 is encoded as

0000 00 00 101 0 0110 0010 0 000 00 10 0010

00A62022

# MIPS encoding example

subu r4, r5, r6

Mnemonic	subu
Description	Subtracts unsigned registers and stores result in a register.
Operation	$rd = rs - rt$
Syntax	subu <i>rd</i> , <i>rs</i> , <i>rt</i>
Encoding	0000 00 ss sss t tttt dddd d 000 00 10 0011

- subu r4, r5, r6 is encoded as

0000 00 00 101 0 0110 0010 0 000 00 10 0011

00A62023

# MIPS encoding example

addi r7, r8, -10

Mnemonic	addi
Description	Signed addition of a register and a sign-extended immediate, stores result in a register.
Operation	$rt = rs + immediate$
Syntax	addi <i>rt</i> , <i>rs</i> , <i>immediate</i>
Encoding	0010 00 <i>ss</i> <i>sss</i> <i>t</i> <i>tttt</i> <i>iiii</i> <i>iiii</i> <i>iiii</i> <i>iiii</i>

- addi r7, r8, -10 is encoded as

0010 00 00 111 0 1000 1111 1111 1111 0110

20E8FF6

# MIPS encoding example

addiu r7, r8, -2

Mnemonic	addiu
Description	Unsigned addition of a register and a sign-extended immediate, stores result in a register.
Operation	$rt = rs + \text{immediate}$
Syntax	addiu <i>rt</i> , <i>rs</i> , <i>immediate</i>
Encoding	0010 01 <i>ss sss t tttt iiii iiii iiii iiii</i>

- addiu r7, r8, -2 is encoded as

0010 01 00 111 0 1000 1111 1111 1111 1110

28E8FFFE

# MIPS encoding example

and r7, r8, r6

Mnemonic	and
Description	Bitwise AND between two registers, stores result in a register
Operation	$rd = rs \& rt$
Syntax	and rd, rs, rt
Encoding	0000 00 ss sss t tttt dddd d 000 00 10 0100

- and r7, r8, r6 is encoded as

0000 00 01 000 0 0110 0011 1 000 00 10 0100

01063824

# MIPS encoding example

`andi r7, r8, -1`

Mnemonic	<code>andi</code>
Description	Bitwise AND between a register and a zero-extended immediate, stores result in register.
Operation	<code>rt = rs &amp; immediate</code>
Syntax	<code>andi rt, rs, immediate</code>
Encoding	<code>0011 00 ss sss t tttt iiii iiii iiii iiii</code>

- `andi r7, r8, -1` is encoded as

`0011 00 01 000 0 0111 0000 0000 1111 1111`  
`310700FF`

# MIPS encoding example

lw r12, 100(r4)

Mnemonic	lw
Description	A word is loaded from memory into a register
Operation	$rt = \text{Mem}[\text{offset} + rs]$
Syntax	lw <i>rt</i> , <i>offset</i> ( <i>rs</i> )
Encoding	1000 11 ss sss t tttt iiii iiii iiii iiii

- lw r12, 100(r4) is encoded as

1000 11 00 100 0 1100 0000 0000 0110 0100

8C8C0064

# MIPS encoding example

sw r12, 100(r4)

Mnemonic	sw
Description	A word is stored from a register into memory
Operation	Mem[ <b>offset</b> + <b>rs</b> ] = <b>rt</b>
Syntax	sw <b>rt</b> , <b>offset</b> ( <b>rs</b> )
Encoding	<b>1010 11 ss sss t tttt iiii iiii iiii iiii</b>

- sw r12, 100(r4) is encoded as

**1010 11 00 100 0 1100 0000 0000 0110 0100**

AC8C0064



# MIPS encoding example

lw r12, -100(r4)

Mnemonic	lw
Description	A word is loaded from memory into a register
Operation	$rt = \text{Mem}[\text{offset} + rs]$
Syntax	lw <i>rt</i> , <i>offset</i> ( <i>rs</i> )
Encoding	1000 11 ss sss t tttt iiii iiii iiii iiii

- lw r12, -100(r4) is encoded as

1000 11 00 100 0 1100 1111 1111 1001 1100

8C8CFF9C

# MIPS encoding example

sw r12, -100(r4)

Mnemonic	sw
Description	A word is stored from a register into memory
Operation	Mem[ <b>offset</b> + <b>rs</b> ] = <b>rt</b>
Syntax	sw <b>rt</b> , <b>offset</b> ( <b>rs</b> )
Encoding	<b>1010 11 ss sss t tttt iiii iiii iiii iiii</b>

- sw r12, -100(r4) is encoded as

**1010 11 00 100 0 1100 1111 1111 1001 1100**

AC8CFF9C

# MIPS encoding example

j 1234

Mnemonic	j
Description	Jump to address
Operation	$PC \leftarrow \text{address}$
Syntax	j address
Encoding	0000 10 ii iiiiiiii iiiiiiii iiiiiiii

- j 1234 is encoded as

0000 10 00 0000 0000 0000 0100 1101 0010

080004D2

# MIPS encoding example

jr r23

Mnemonic	jr
Description	Jump to address in register
Operation	$PC \leftarrow rs$
Syntax	jr rs
Encoding	0000 00 ss sss 0 0000 0000 0000 0000 1000

- jr r23 is encoded as

0000 00 10 111 0 0000 0000 0000 0000 1000

# Custom MIPS design

- We will begin to design the Microarchitecture ( $\mu A$ ) for each stage of a custom MIPS  $\mu P$ .
- We will use an incremental approach, *i.e.*, basic features will be improved over time.
- We will focus on single-cycle design at first.

- We will divide our MIPS into R-, I- and J-Type instructions.
- We will start by implementing R-Type instructions.
- I- and J-Type instructions will be added incrementally.
- We will analyse the necessary datapath for implementing each instruction type.

## General design specifications

- Instruction set based (but modified) on 16-bit MIPS  $\mu$ P.
- Single-cycle design.
- Data width is 16-bits.
- Instruction encoding (instruction width) is 32-bits long.
- RF contains 32 registers.
  - **r0 must** always be 0, *i.e.*, r0 is not writeable. Useful for load and store operations.
  - **r31** is return address. More about this later.



# PC datapath

# PC datapath

- Program Counter (PC) indicates the instruction being executed.
- PC is effectively the read address of IM.
- PC **updates** its value every clock cycle.

 


Figure 7: Basic PC datapath.

## R-Type datapath

# Custom MIPS design

- R-Type instructions are instructions in which ALU operands are retrieved from RF and result is stored back in RF as well.

Instruction	Syntax	Meaning
ADD	ADD rd, rs, rt	$\text{Reg}[\text{rd}] \leftarrow \text{Reg}[\text{rs}] + \text{Reg}[\text{rt}]$
SUB	SUB rd, rs, rt	$\text{Reg}[\text{rd}] \leftarrow \text{Reg}[\text{rs}] - \text{Reg}[\text{rt}]$
NAND	NAND rd, rs, rt	$\text{Reg}[\text{rd}] \leftarrow \sim(\text{Reg}[\text{rs}] \& \text{Reg}[\text{rt}])$
NOR	NOR rd, rs, rt	$\text{Reg}[\text{rd}] \leftarrow \sim(\text{Reg}[\text{rs}]   \text{Reg}[\text{rt}])$
XNOR	XNOR rd, rs, rt	$\text{Reg}[\text{rd}] \leftarrow \sim(\text{Reg}[\text{rs}] \wedge \text{Reg}[\text{rt}])$
AND	AND rd, rs, rt	$\text{Reg}[\text{rd}] \leftarrow \text{Reg}[\text{rs}] \& \text{Reg}[\text{rt}]$
OR	OR rd, rs, rt	$\text{Reg}[\text{rd}] \leftarrow \text{Reg}[\text{rs}]   \text{Reg}[\text{rt}]$
XOR	XOR rd, rs, rt	$\text{Reg}[\text{rd}] \leftarrow \text{Reg}[\text{rs}] \wedge \text{Reg}[\text{rt}]$
SLL	SLL rd, rs, sa	$\text{Reg}[\text{rd}] \leftarrow \text{Reg}[\text{rs}] \ll \text{sa}$
SRL	SRL rd, rs, sa	$\text{Reg}[\text{rd}] \leftarrow \text{Reg}[\text{rs}] \gg \text{sa}$
SLA	SLA rd, rs, sa	$\text{Reg}[\text{rd}] \leftarrow \text{Reg}[\text{rs}] \ll \text{sa}$
SRA	SRA rd, rs, sa	$\text{Reg}[\text{rd}] \leftarrow \text{Reg}[\text{rs}] \gg \text{sa}$

# R-Type arithmetic/logic instruction

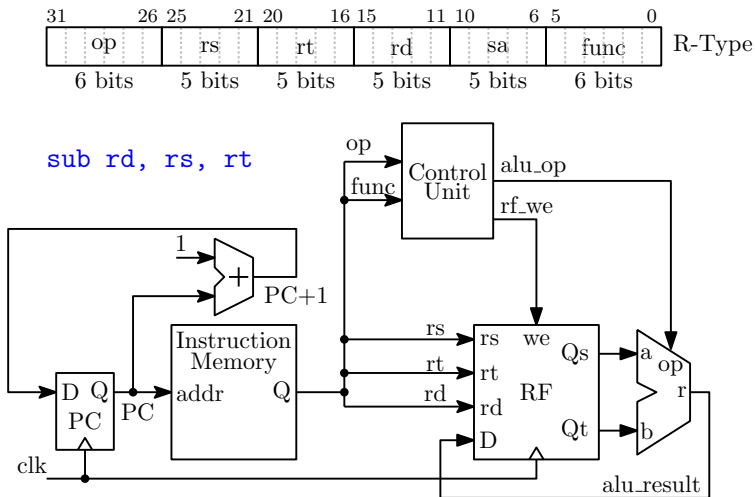


Figure 8:  $\mu$ A of MIPS R-Type arithmetic/logic instructions datapath.

# R-Type arithmetic/logic instructions datapath

- Arithmetic and Logic Unit (ALU) takes its operands `a` and `b` from outputs `Qs` and `Qt` from RF, respectively.
- Control unit asserts `alu_op` according to value of `func` in order to instruct ALU the type of operation to be performed, *i.e.*, `add`, `sub`, `and`, *etc.*
- Control unit asserts `rf_we` in order to write the `alu_result` back into RF.

# R-Type shift instructions datapath

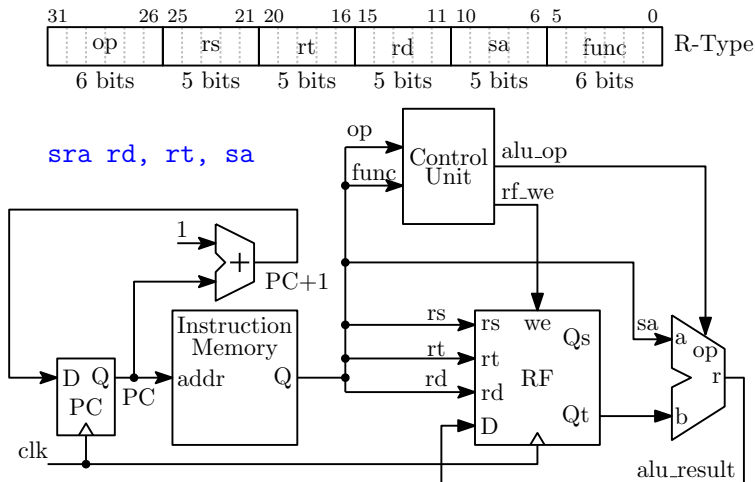


Figure 9:  $\mu$ A of MIPS R-Type shift instructions datapath.

# R-Type shift instructions

- Input `a` in ALU represents shift amount `sa`.
- `sa` must be zero-extended.
- `rs` and `Qs` are not used.



# R-Type instructions datapath

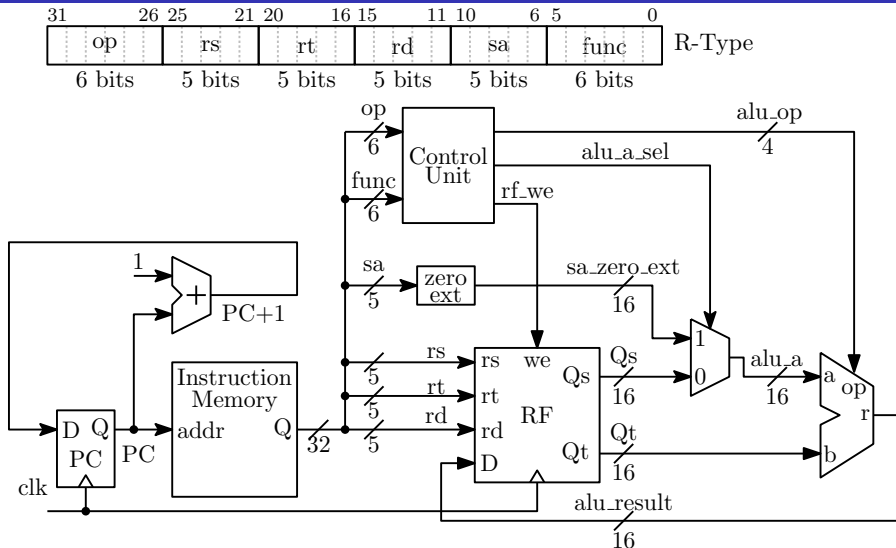


Figure 10:  $\mu A$  of MIPS R-Type instructions datapath.

# I-Type datapath

# I-Type arithmetic/logic instructions datapath

- I-Type instructions use immediate addressing mode.

Instruction	Syntax	Meaning
ADDI	ADDI rt, rs, imm	$\text{Reg[rt]} \leftarrow \text{Reg[rs]} + \text{imm}$
SUBI	SUBI rt, rs, imm	$\text{Reg[rt]} \leftarrow \text{Reg[rs]} - \text{imm}$
ANDI	ANDI rt, rs, imm	$\text{Reg[rt]} \leftarrow \text{Reg[rs]} \& \text{imm}$
ORI	ORI rt, rs, imm	$\text{Reg[rt]} \leftarrow \text{Reg[rs]}   \text{imm}$
XORI	XORI rt, rs, imm	$\text{Reg[rt]} \leftarrow \text{Reg[rs]} \wedge \text{imm}$
LUI	LUI rt, imm	$\text{Reg[rt]} \leftarrow \{\text{imm}[7:0], 8'b0\}$
LLI	LLI rt, imm	$\text{Reg[rt]} \leftarrow \{8'b0, \text{imm}[7:0]\}$
LW	LW rt, imm(rs)	$\text{Reg[rt]} \leftarrow \text{Mem[rs+imm]}$
SW	SWR rt, imm(rs)	$\text{Mem[rs+imm]} \leftarrow \text{Reg[rt]}$
BEQ	BEQ rt, rs, imm	if ( $\text{Reg[rt]} == \text{Reg[rs]}$ ) then $\text{PC} \leftarrow \text{imm}$
BNE	BNE rt, rs, imm	if ( $\text{Reg[rt]} != \text{Reg[rs]}$ ) then $\text{PC} \leftarrow \text{imm}$

# I-Type arithmetic/logic instructions datapath

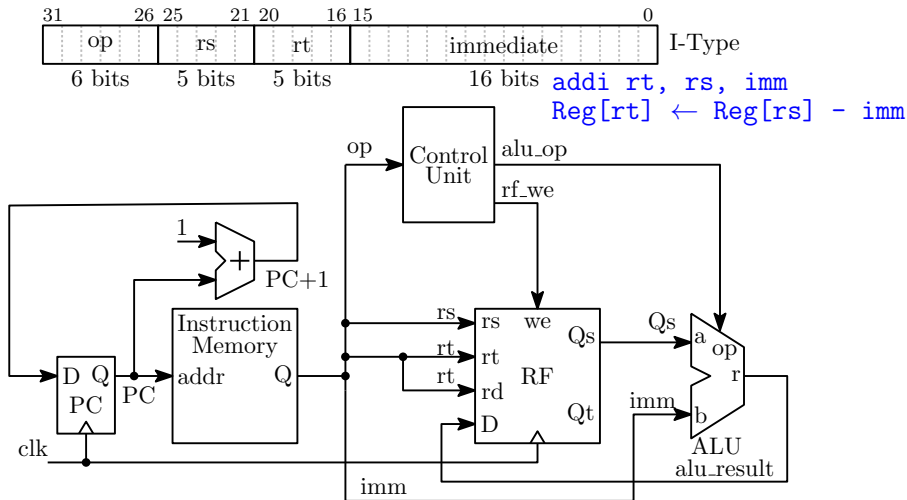


Figure 11:  $\mu A$  of a MIPS I-Type arithmetic/logic instruction.

# I-Type load instructions datapath

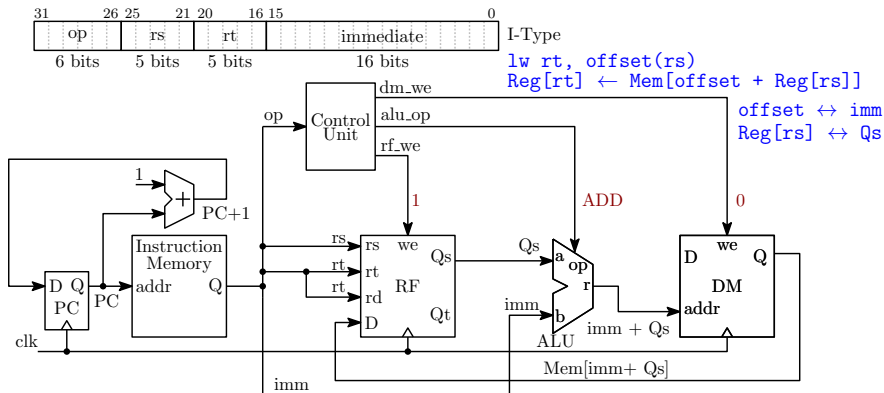


Figure 12:  $\mu A$  of a MIPS I-Type load instruction datapath.

# I-Type store instructions datapath

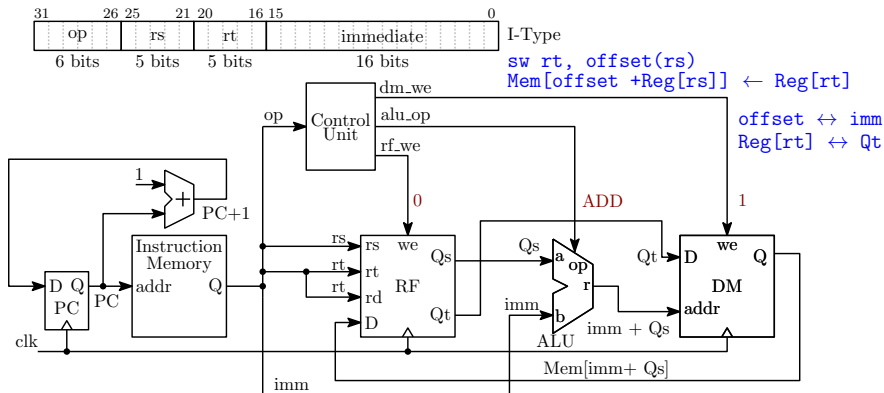


Figure 13:  $\mu A$  of a MIPS I-Type store instruction datapath.

# I-Type load/store instructions

- ALU will perform calculations in order to find the displacement address to read/write data from/to.
  - `lw rt, offset(rs)` is equivalent to
$$\text{Reg[rt]} \leftarrow \text{Mem}[\text{offset} + \text{Reg[rs]}]$$
  - `sw rt, offset(rs)` is equivalent to
$$\text{Mem}[\text{offset} + \text{Reg[rs]}] \leftarrow \text{Reg[rt]}$$
- Control unit provides a `dm_we` signal, which is a write enable for reading/writing from DM.

# I-Type conditional branch instructions

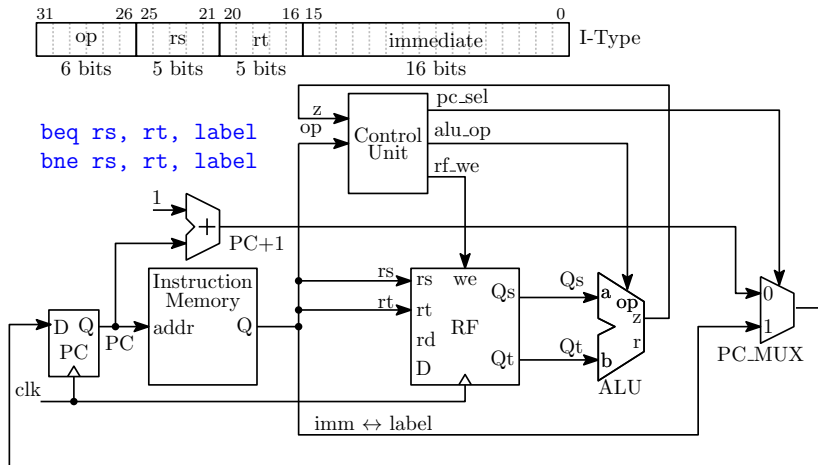


Figure 14:  $\mu$ A of a MIPS I-Type conditional branch instruction.



# I-Type load/store instructions

- Contents of **rs** and **rt** are compared in order to determine whether to branch or not.
- If the branch is taken, PC is updated with an **imm** value, which is the target address.
- There is no write-back to RF.

## J-Type datapath

# J-Type instructions

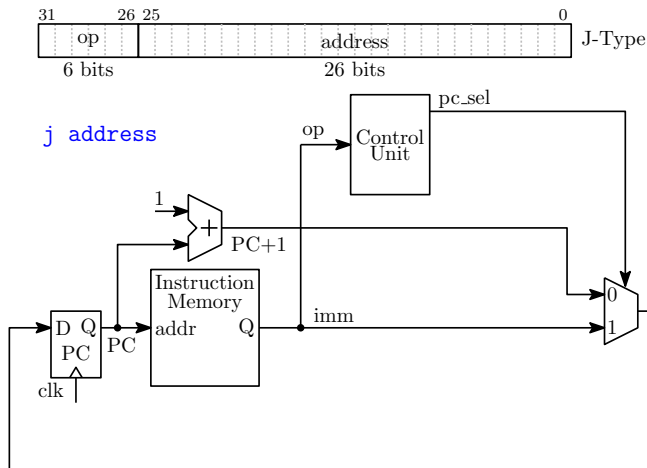


Figure 15:  $\mu A$  of a MIPS J-Type jump instruction.