

# TC2009B: Digital design Multiplication and Division

Isaac Pérez Andrade

ITESM Guadalajara  
School of Engineering & Science  
Department of Computer Science  
August – December 2021



# References

The following material has been adopted and adapted from

Patterson, D. A., Hennessy, J. L., *Computer Organization and design: The hardware/software interface – ARM edition*, Morgan Kaufmann, 2017.

S. L. Harris and D. M. Harris, *Digital design and computer architecture - ARM edition*, Morgan Kaufmann, 2016.

# Arithmetic for Computers

## Operations on integers

- Addition and subtraction
- Multiplication and division
- Dealing with overflow

## Floating-point real numbers

- Representation and operations

# Integer operations

# Two's complement review

Assume two's complement format

- Q: What's the range (minimum and maximum values that can be represented) of an  $N$ -bit two's complement number?

A:  $[-(2^{(N-1)}), 2^{(N-1)} - 1]$

- For example, an 8-bit two's complement number may represent values in the range

$$[-2^{8-1}, 2^{8-1} - 1] = [-2^7, 2^7 - 1] = [-128, 127]$$

# Overflow & underflow

- Q: What is **overflow**?

A: A condition when the result of a calculation **exceeds** the **maximum** value that can be represented in a numeric format.

- Q: What is **underflow**?


A: A condition when the result of a calculation is **smaller** than the **minimum** value that can be represented in a numeric format.

- Sometimes, the term overflow is used for describing both conditions.

# Addition

# Integer addition

Example:  $7 + 6$

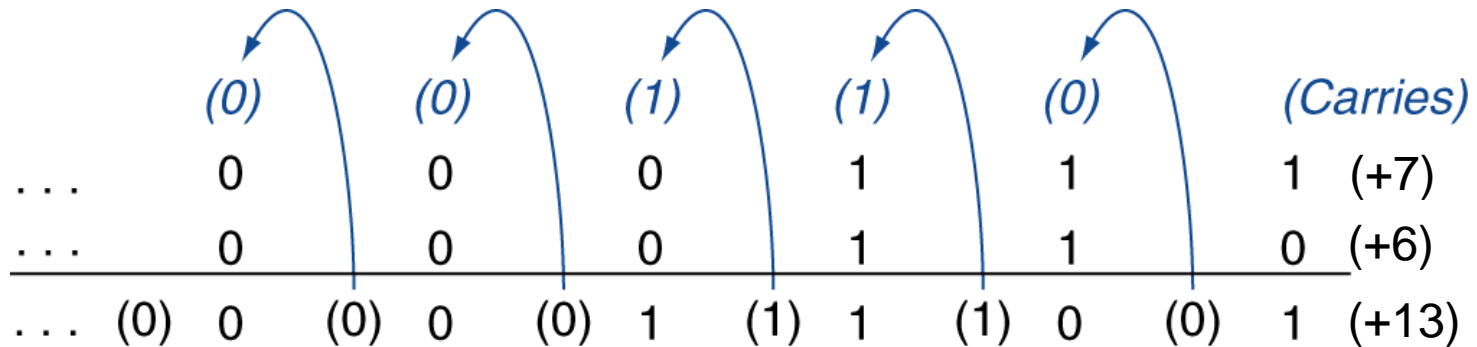

Overflow if result out of range

- Adding +ve and -ve operands, no overflow
- Adding two +ve operands  
Overflow if result sign is 1
- Adding two -ve operands  
Overflow if result sign is 0



# Integer addition

- Example: Adding two 4-bit two's complement numbers

$$5 + 1$$

$$\begin{array}{r} +5: \quad 0101 \\ +1: \quad 0001 \\ \hline +6: \quad 0110 \end{array}$$

$$-2 + 5$$

$$\begin{array}{r} -2: \quad 1110 \\ +5: \quad 0101 \\ \hline +3: \quad 0011 \end{array}$$

$$3 + 6$$

$$\begin{array}{r} +3: \quad 0011 \\ +6: \quad 0110 \\ \hline -7: \quad 1001 \end{array}$$


$$-7 + (-1)$$

$$\begin{array}{r} -7: \quad 1001 \\ -1: \quad 1111 \\ \hline -8: \quad 1000 \end{array}$$

$$-3 + (-6)$$

$$\begin{array}{r} -3: \quad 1101 \\ -6: \quad 1010 \\ \hline +7: \quad 0111 \end{array}$$

Overflow: +9 and -9  
can not be represented in 4-bit  
two's complement.



# Subtraction

# Integer subtraction

Addition with negation of second operand

Example:  $7 - 6 = 7 + (-6)$

$$\begin{array}{r} +7: \quad 0000 \ 0000 \ \dots \ 0000 \ 0111 \\ -6: \quad 1111 \ 1111 \ \dots \ 1111 \ 1010 \\ \hline +1: \quad 0000 \ 0000 \ \dots \ 0000 \ 0001 \end{array}$$

- Overflow if result out of range
  - Subtracting two +ve or two -ve operands, no overflow
  - Subtracting +ve from -ve operand
    - Overflow if result sign is 0
  - Subtracting -ve from +ve operand
    - Overflow if result sign is 1

# Integer subtraction

- Example: Subtracting two 4-bit two's complement numbers

$$5 - (+1)$$

$$\begin{array}{r} +5: \quad 0101 \\ -1: \quad 1111 \\ \hline +4: \quad 0100 \end{array}$$

$$-2 - (-5)$$

$$\begin{array}{r} -2: \quad 1110 \\ +5: \quad 0101 \\ \hline +3: \quad 0011 \end{array}$$

$$-3 - (+6)$$

$$\begin{array}{r} -3: \quad 1101 \\ -6: \quad 1010 \\ \hline +7: \quad 0111 \end{array}$$

$$7 - (-1)$$

$$\begin{array}{r} +7: \quad 0111 \\ +1: \quad 0001 \\ \hline -8: \quad 1000 \end{array}$$

Overflow: -9 and +8 can not be represented in 4-bit two's complement.



# Addition & subtraction overflow summary

- Overflow conditions for additions and subtraction in two's complement.

Operation	Operand A	Operand B	Result indicating overflow
$A + B$	$\geq 0$	$\geq 0$	$< 0$
$A + B$	$< 0$	$< 0$	$\geq 0$
$A - B$	$\geq 0$	$< 0$	$< 0$
$A - B$	$< 0$	$\geq 0$	$\geq 0$

# Multiplication

# Multiplier

- **Partial products** formed by multiplying a single digit of the multiplier with multiplicand
- **Shifted** partial products **summed** to form result

## Decimal

$$\begin{array}{r} 230 \\ \times 42 \\ \hline 460 \\ + 920 \\ \hline 9660 \end{array}$$

multiplicand  
multiplier  
partial  
products  
result

$$230 \times 42 = 9660$$

## Binary

$$\begin{array}{r} 0101 \\ \times 0111 \\ \hline 0101 \\ 0101 \\ 0101 \\ + 0000 \\ \hline 0100011 \end{array}$$

$$5 \times 7 = 35$$


# Parallel multiplication

$$\begin{array}{r}
 \begin{array}{cccc}
 & A_3 & A_2 & A_1 & A_0 \\
 \times & B_3 & B_2 & B_1 & B_0 \\
 \hline
 & A_3B_0 & A_2B_0 & A_1B_0 & A_0B_0 \\
 & A_3B_1 & A_2B_1 & A_1B_1 & A_0B_1 \\
 & A_3B_2 & A_2B_2 & A_1B_2 & A_0B_2 \\
 + & A_3B_3 & A_2B_3 & A_1B_3 & A_0B_3 \\
 \hline
 P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}
 \end{array}$$


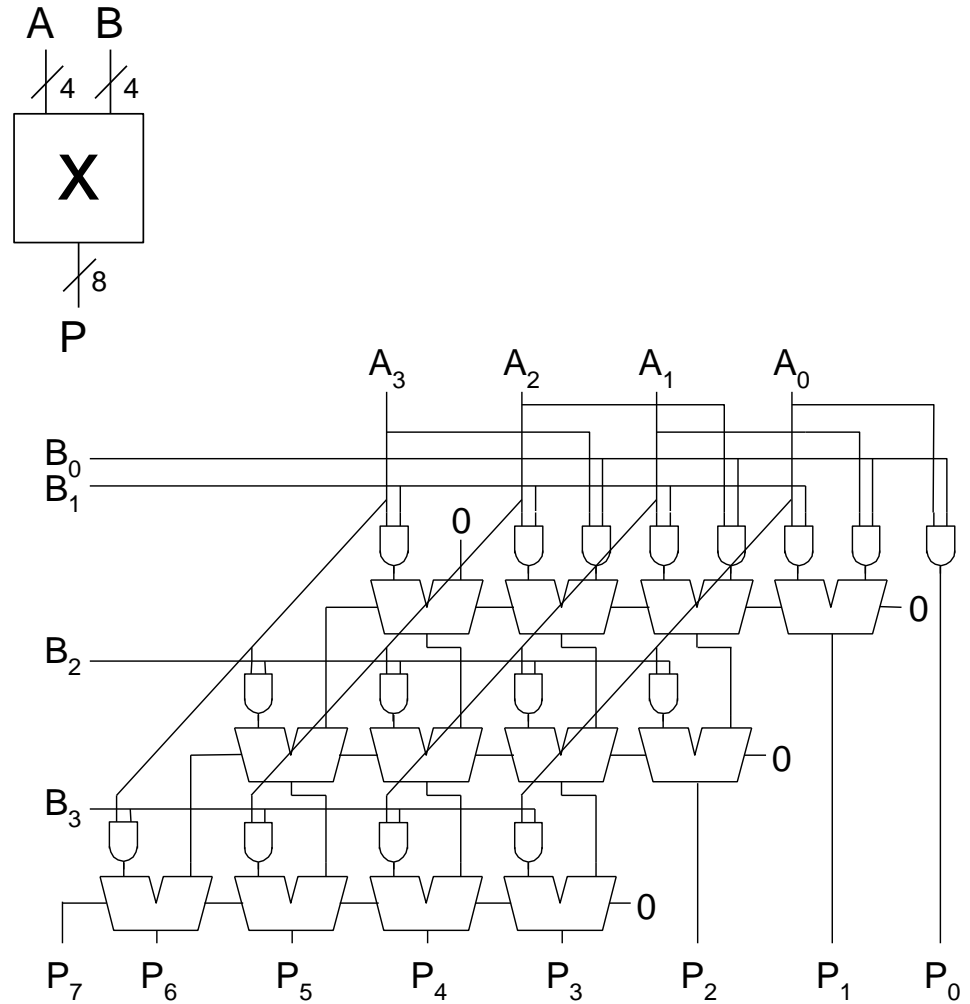
# Parallel multiplication


$$\begin{array}{r}
 \begin{array}{cccc}
 & A_3 & A_2 & A_1 & A_0 \\
 \times & B_3 & B_2 & B_1 & B_0 \\
 \hline
 & A_3B_0 & A_2B_0 & A_1B_0 & A_0B_0 \\
 & A_3B_1 & A_2B_1 & A_1B_1 & A_0B_1 \\
 & A_3B_2 & A_2B_2 & A_1B_2 & A_0B_2 \\
 + & A_3B_3 & A_2B_3 & A_1B_3 & A_0B_3 \\
 \hline
 P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}
 \end{array}$$


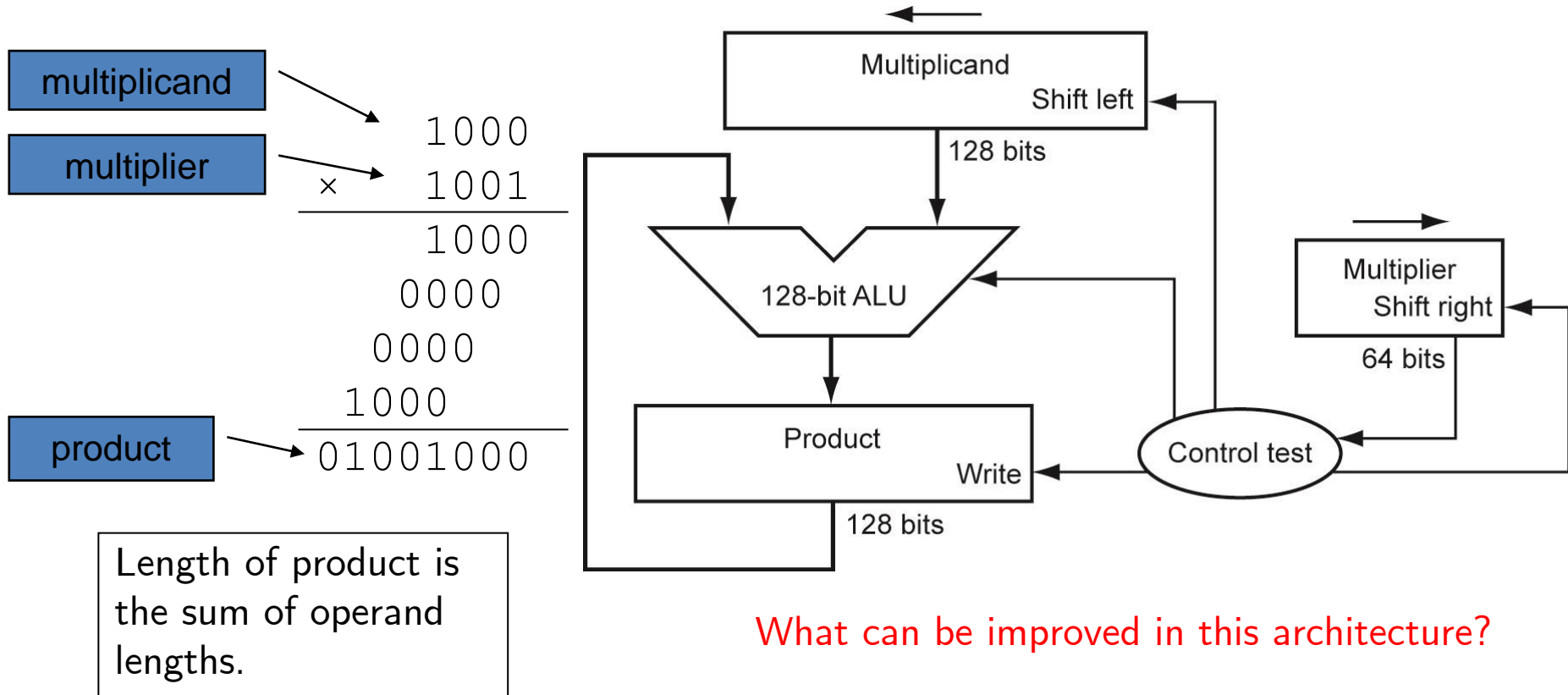
# Sequential multiplication

- Start with long-multiplication approach

Assume we want to multiply two 64-bit numbers




What can be improved in this architecture?


$$A_{M\text{-bits}} \times B_{N\text{-bits}} = X_{(M+N)\text{-bits}}$$
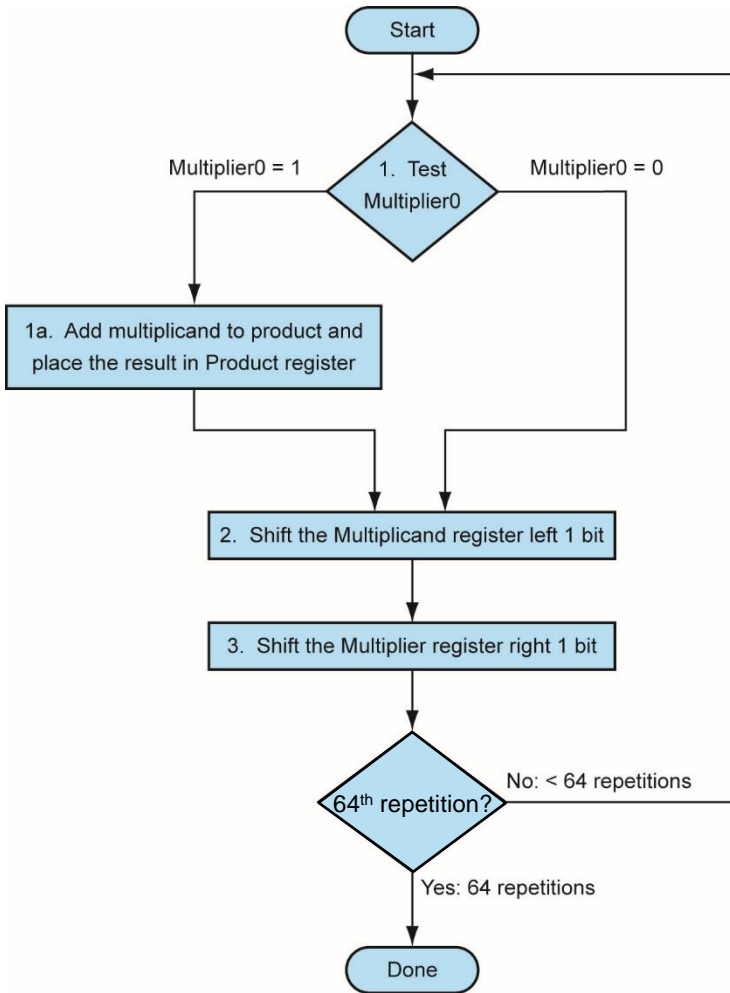
# Multiplication hardware

There's one error in the flow chart. Can you spot it?




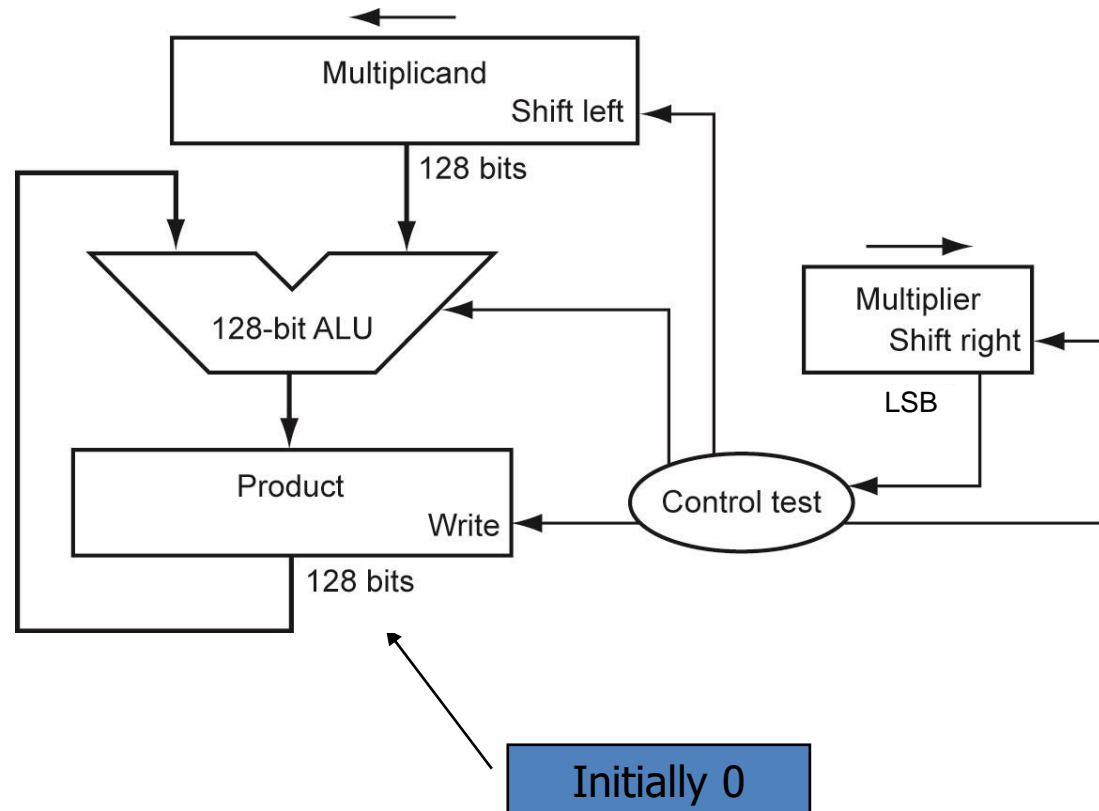What can be improved in this architecture?


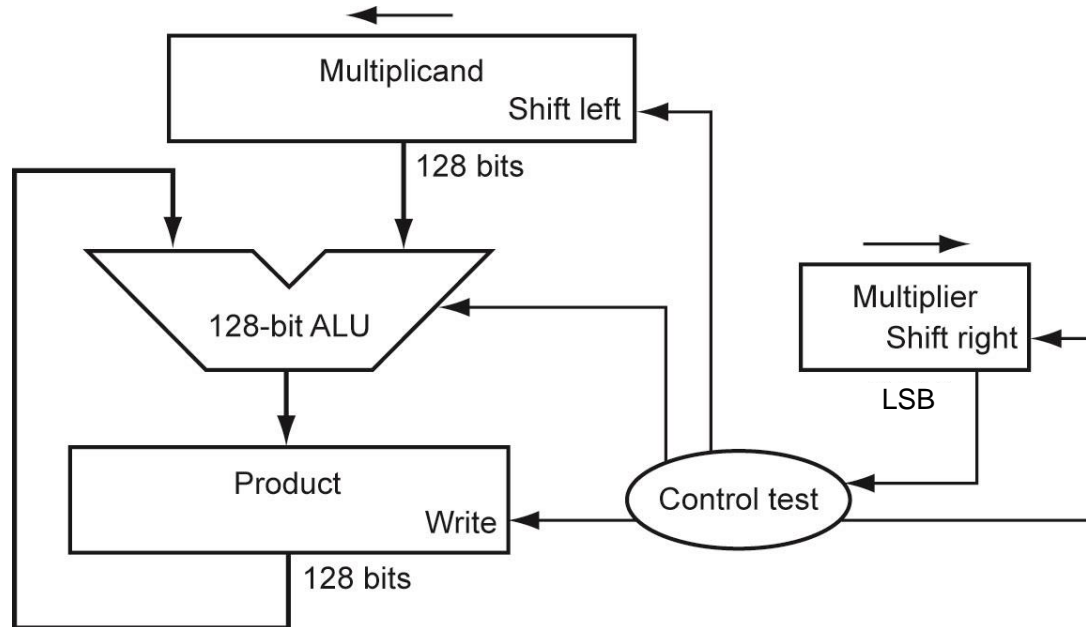
# Multiplication hardware

This architecture has a major flaw.  
Can you spot it?




For multiplying two N-bit number, it requires:

- Two  $2N$ -bit registers
- One  $N$ -bit register
- A  $2N$ -bit ALU

**This is a waste of resources!**

# Optimised multiplier

- Perform steps in parallel: add/shift

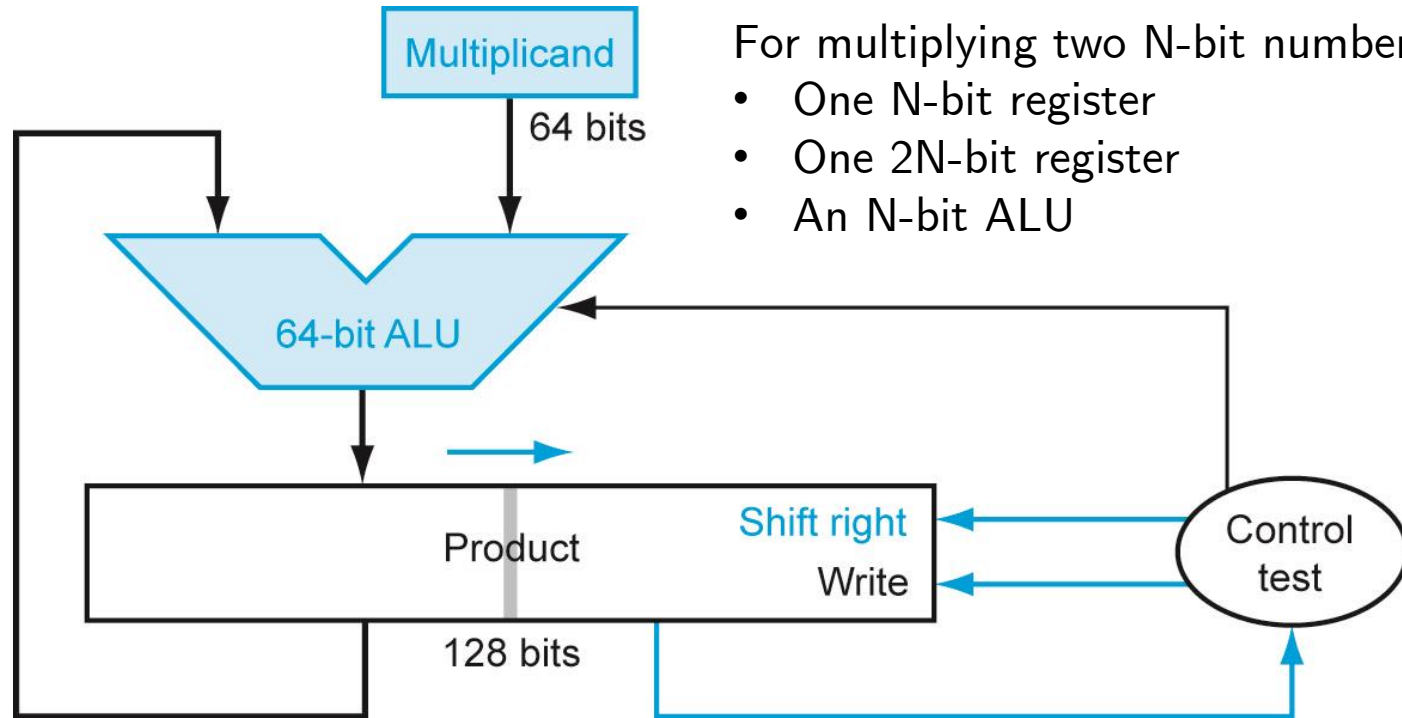



For multiplying two N-bit number, it requires:

- One N-bit register
- One 2N-bit register
- An N-bit ALU

One cycle per partial-product addition


- That's ok, if frequency of multiplications is low

# Optimised multiplier

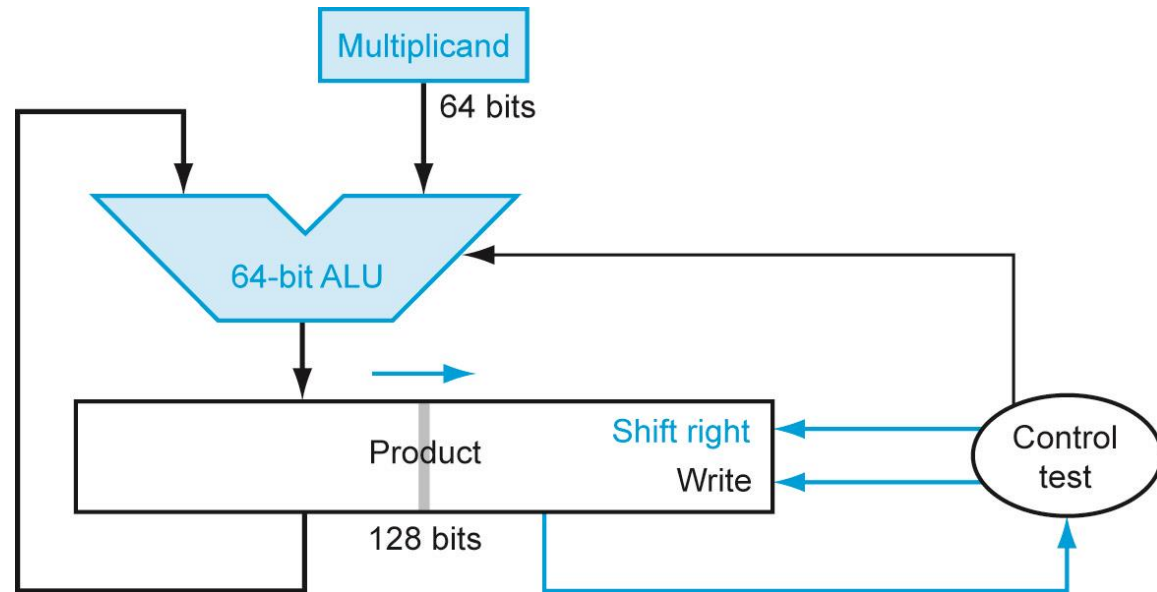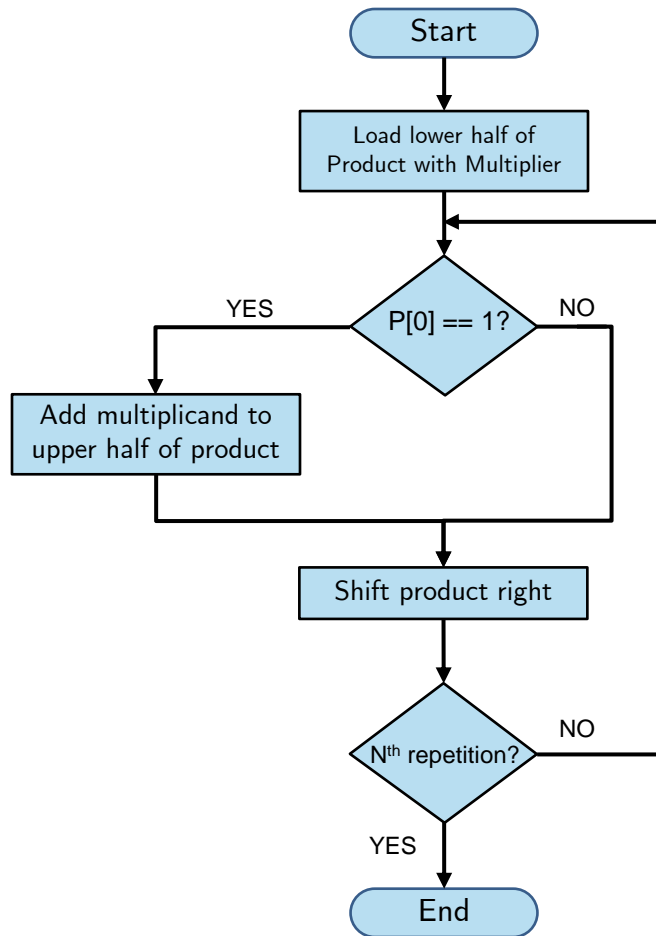

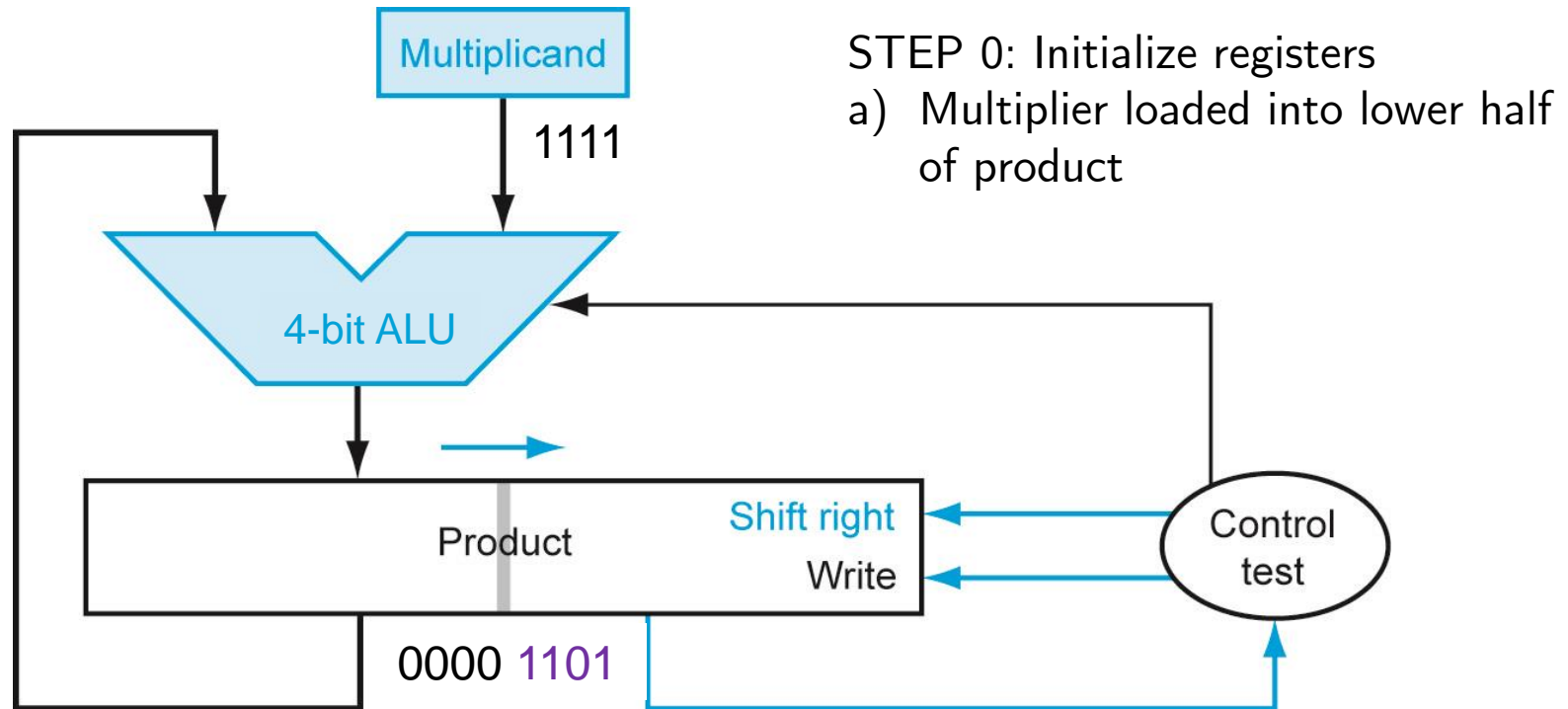
# Optimised multiplier - example

- Multiplicand =  $15_{10}$ : 1111
- Multiplier =  $13_{10}$ : 1101


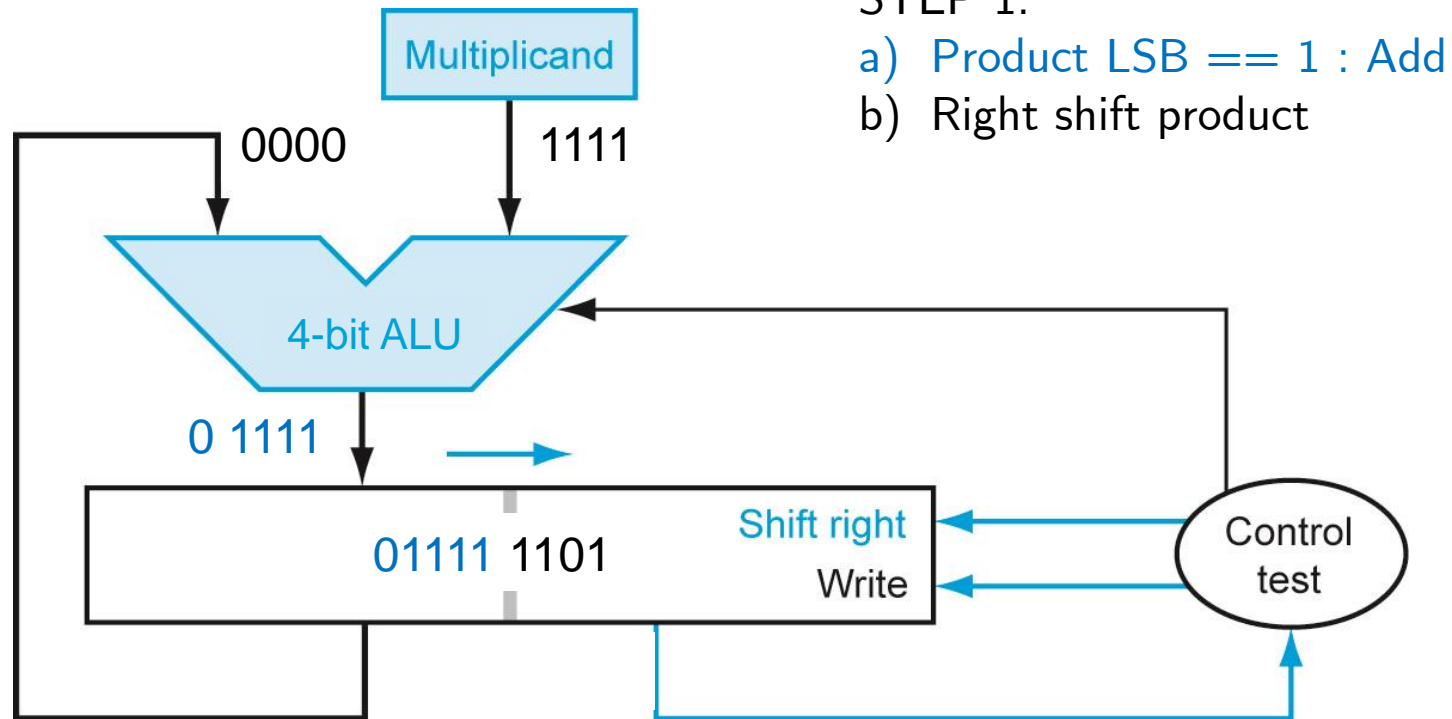
# Optimised multiplier - example


- Multiplicand =  $15_{10}$ : 1111
- Multiplier =  $13_{10}$ : 1101





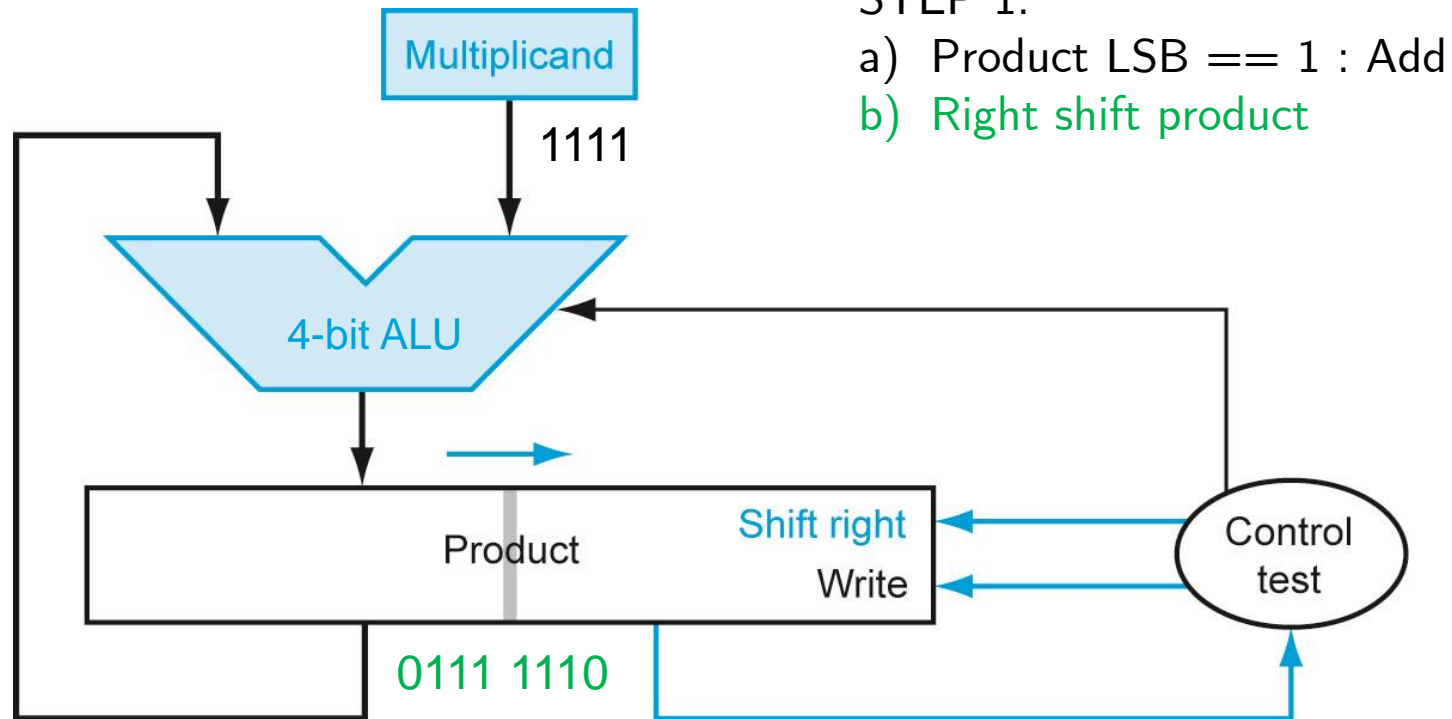
# Optimised multiplier - example

- Multiplicand =  $15_{10}$ : 1111
- Multiplier =  $13_{10}$ : 1101


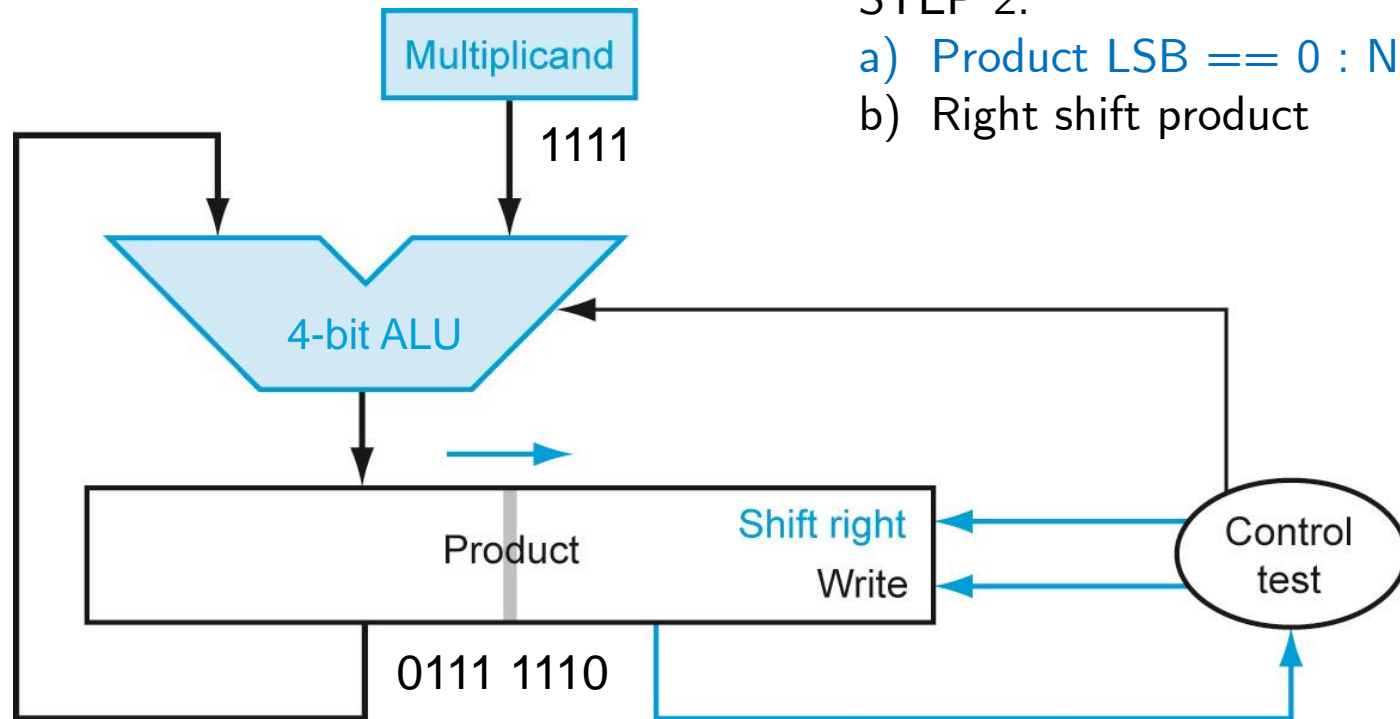
# Optimised multiplier - example

- Multiplicand =  $15_{10}$ : 1111
- Multiplier =  $13_{10}$ : 1101




STEP 2:

- a) Product LSB == 0 : No Add
- b) Right shift product
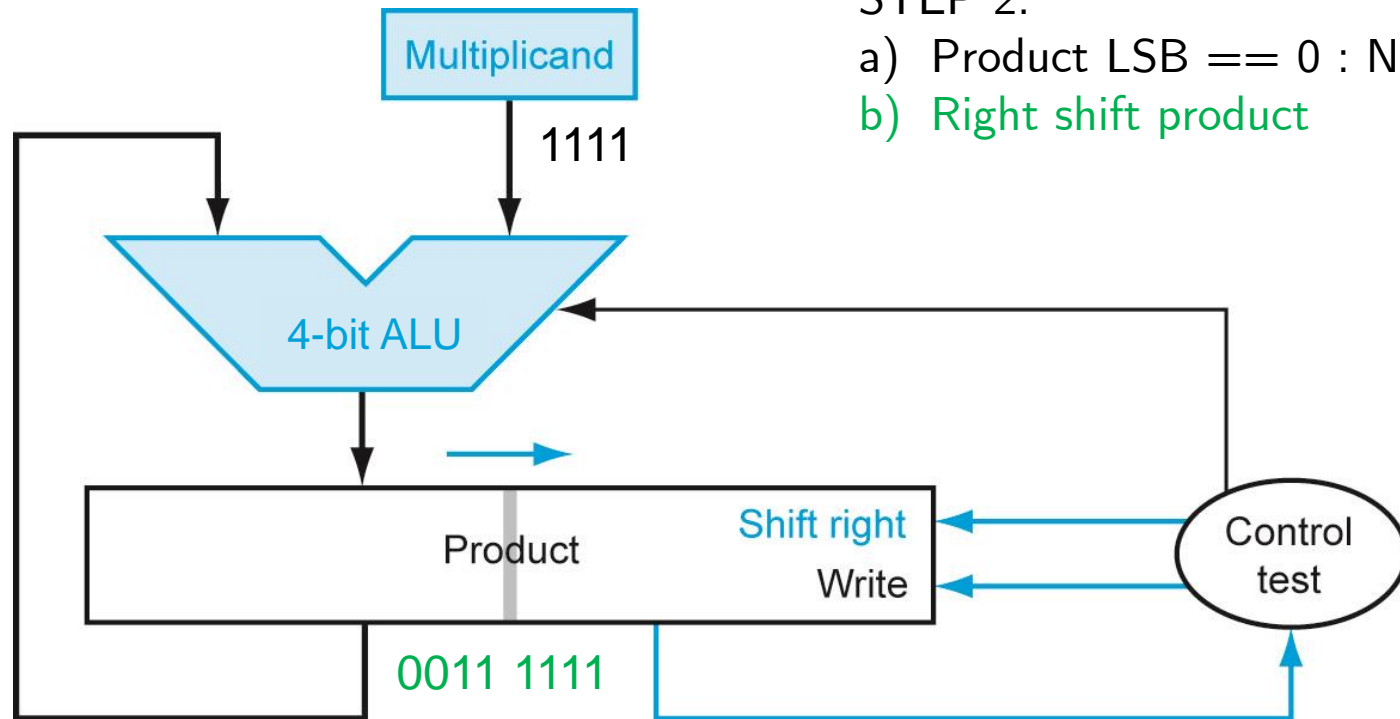
# Optimised multiplier - example

- Multiplicand =  $15_{10}$ : 1111
- Multiplier =  $13_{10}$ : 1101




STEP 2:

a) Product LSB == 0 : No Add

b) Right shift product

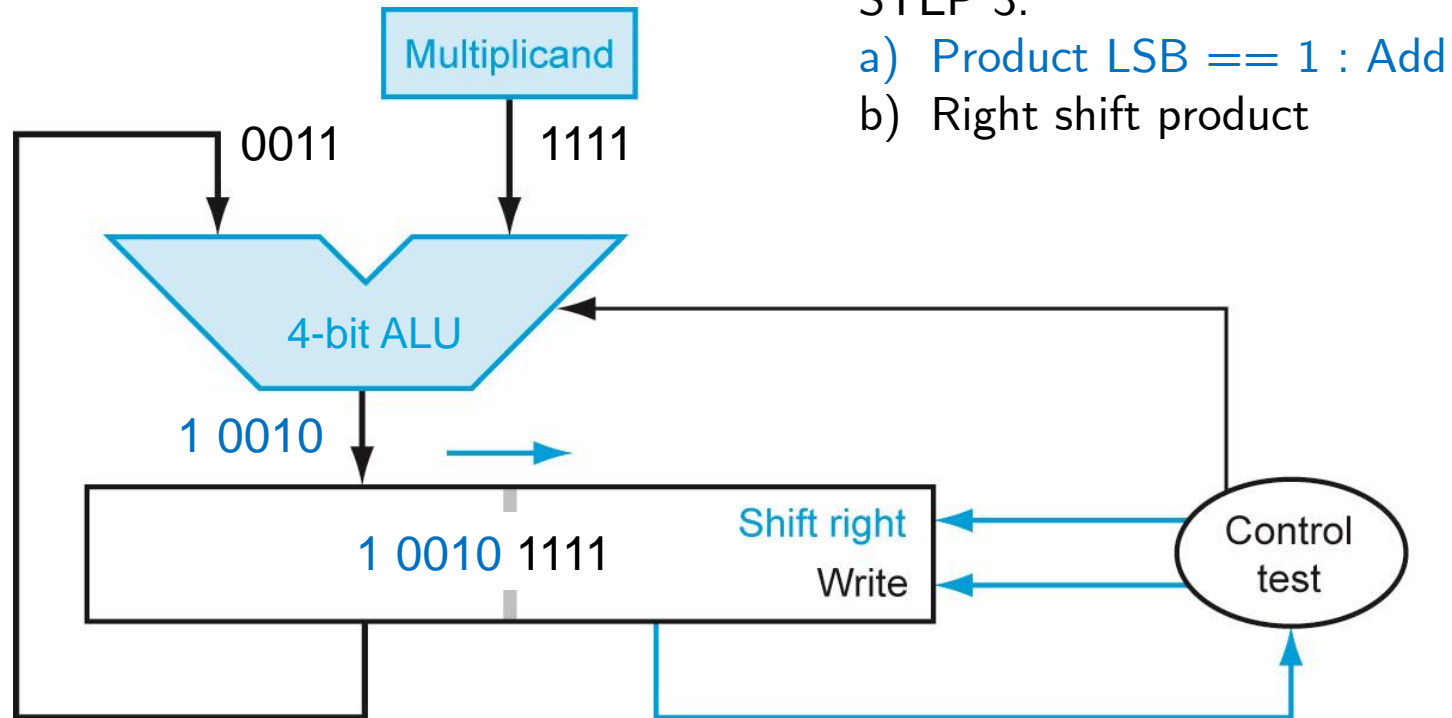
# Optimised multiplier - example

- Multiplicand =  $15_{10}$ : 1111
- Multiplier =  $13_{10}$ : 1101



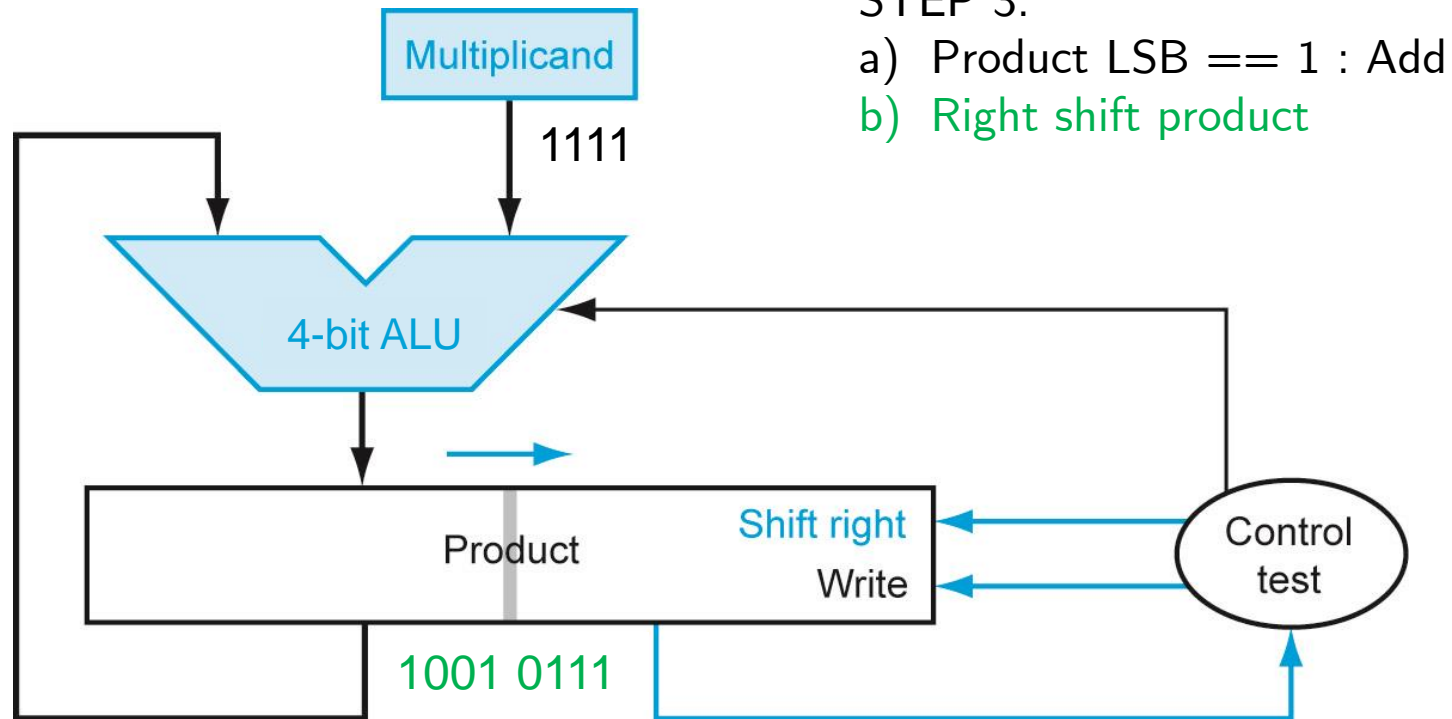
# Optimised multiplier - example

- Multiplicand =  $15_{10}$ : 1111
- Multiplier =  $13_{10}$ : 1101



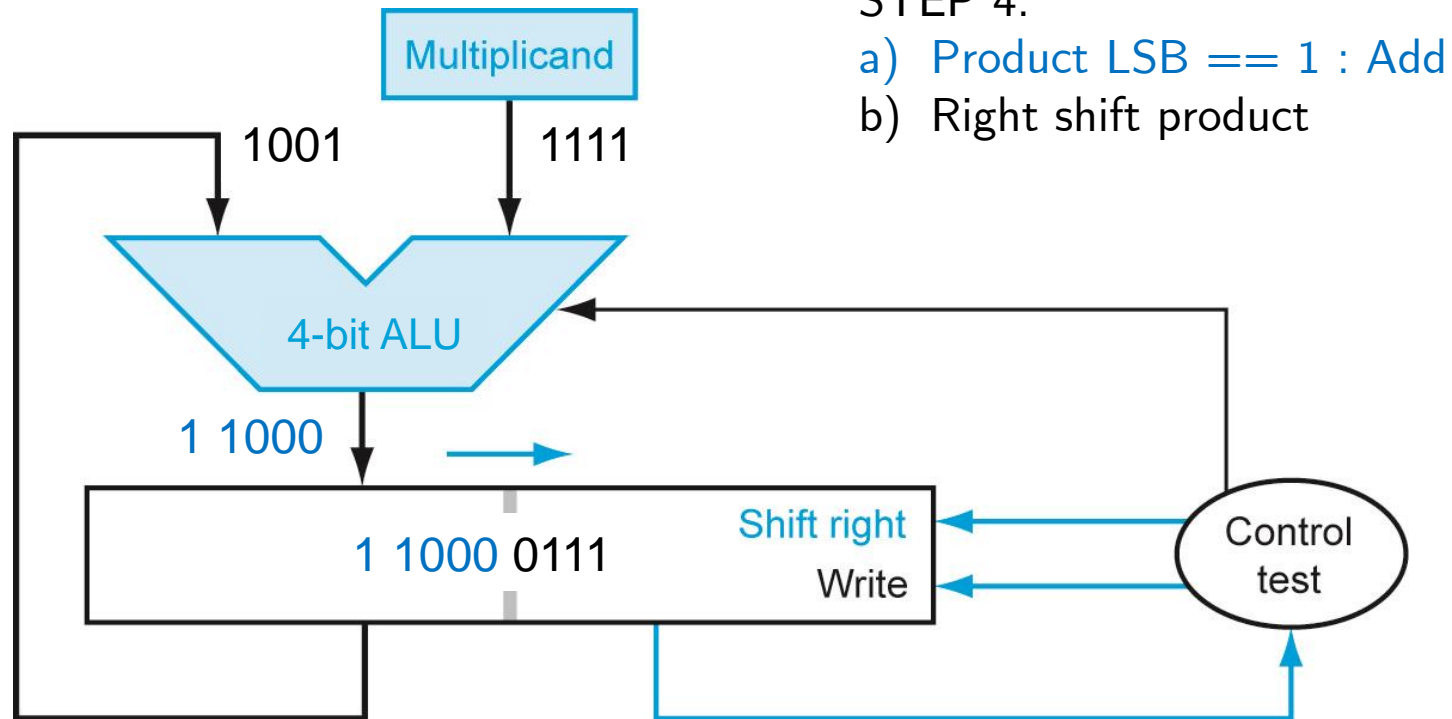
# Optimised multiplier - example

- Multiplicand =  $15_{10}$ : 1111
- Multiplier =  $13_{10}$ : 1101



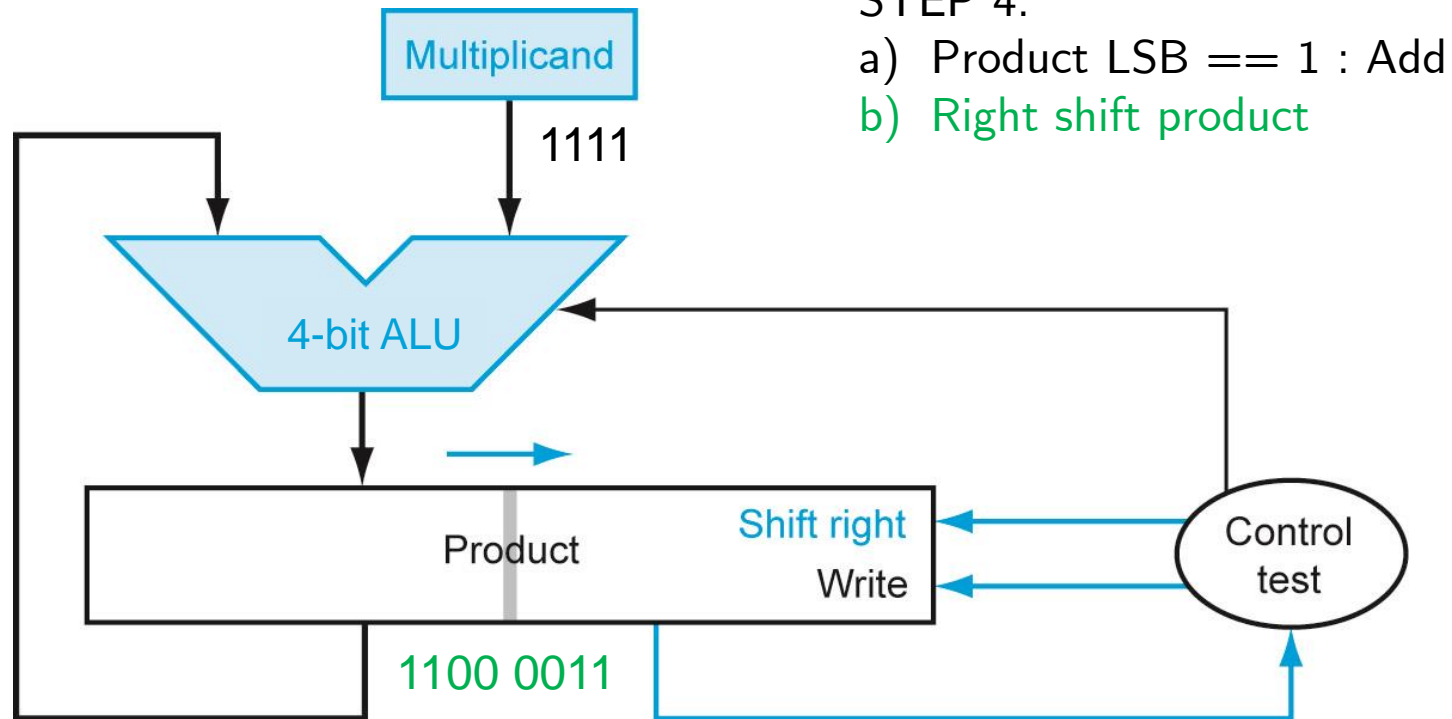
# Optimised multiplier - example

- Multiplicand =  $15_{10}$ : 1111
- Multiplier =  $13_{10}$ : 1101


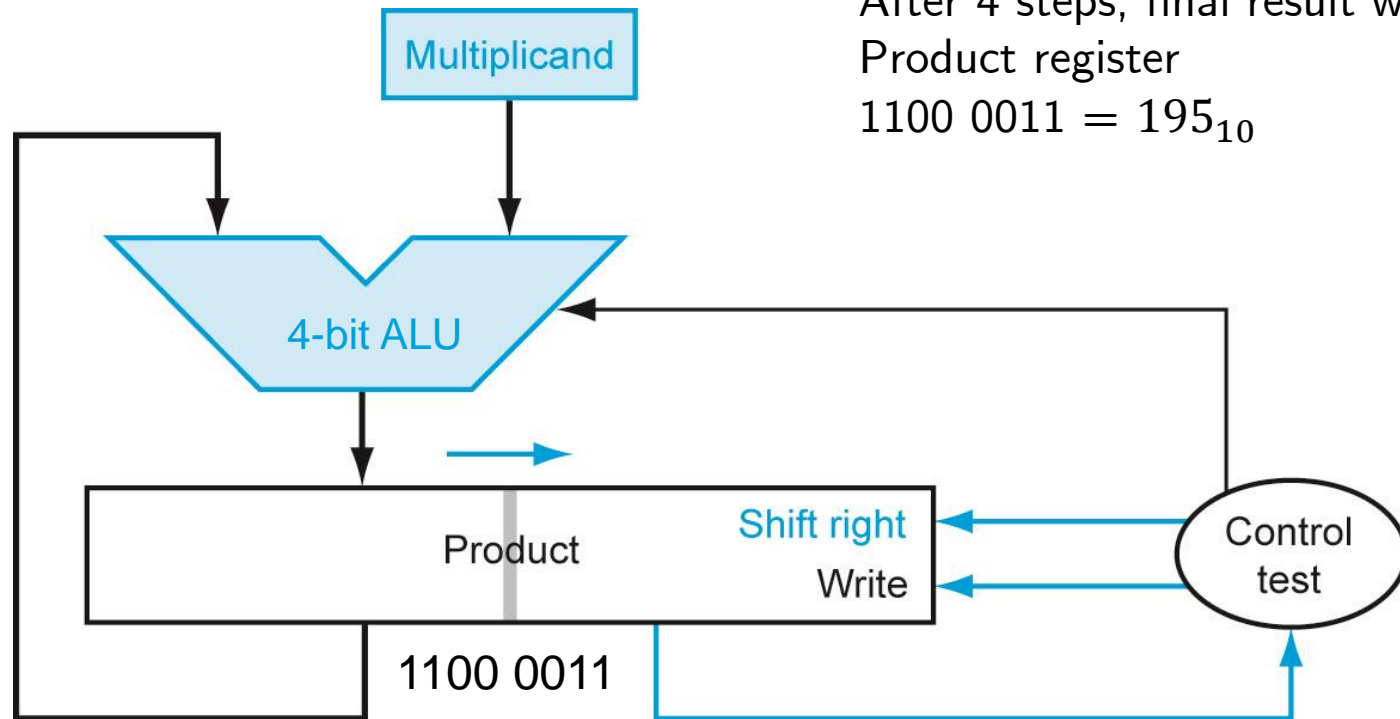
# Optimised multiplier - example

- Multiplicand =  $15_{10}$ : 1111
- Multiplier =  $13_{10}$ : 1101






# Signed multiplication

- So far, we've only dealt with unsigned operands.
- What happens in signed multiplication?
- For adding two signed N-bit numbers:
  1. Convert both multiplicand and multiplier to positive numbers and keep track of their respective sign.
  2. Apply multiplication algorithm N-1 times.
  3. Negate product if signs are not the same.
- Alternatively, previous algorithm works for signed numbers if shifts are performed using sign extension.

# Division

# Division

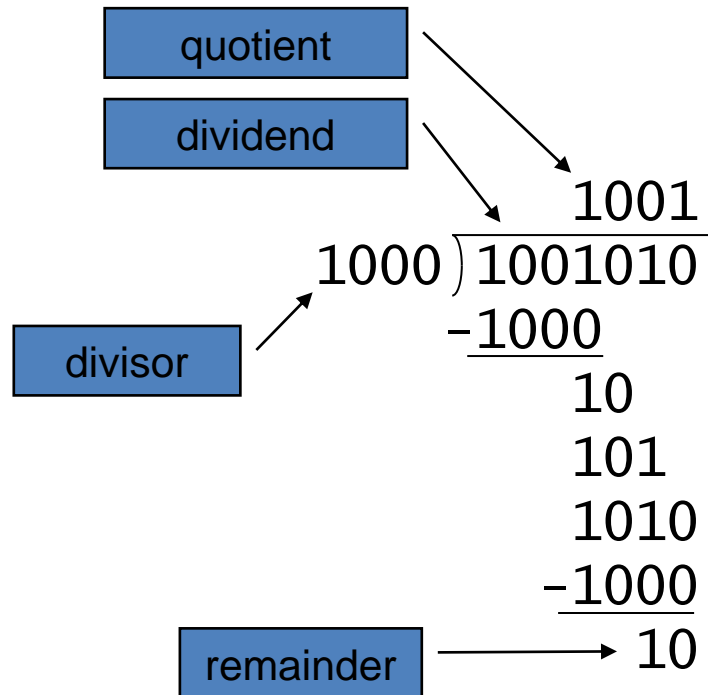

*n*-bit operands yield *n*-bit quotient and remainder

- Check for 0 divisor
- Long division approach
  - If divisor  $\leq$  dividend bits
    - 1 bit in quotient, subtract
  - Otherwise
    - 0 bit in quotient, bring down next dividend bit
- Restoring division
  - Do the subtract, and if remainder goes  $< 0$ , add divisor back
- Signed division
  - Divide using absolute values
  - Adjust sign of quotient and remainder as required

# Divider

$$A/B = Q + R$$

**Decimal Example:**  $2584/15 = 172 \text{ R}4$

**Long-Hand:**

$$\begin{array}{r} 172 \text{ R}4 \\ 15 \overline{) 2584} \\ \underline{-15} \phantom{00} \\ 108 \phantom{00} \\ \underline{-105} \phantom{00} \\ 34 \phantom{00} \\ \underline{-30} \phantom{00} \\ 4 \end{array}$$

$$\begin{array}{r} 0002 \\ -15 \\ \hline -13 \end{array} \quad \begin{array}{r} 0 \\ 3 \end{array} \begin{array}{r} \phantom{0} \\ 2 \end{array} \begin{array}{r} \phantom{0} \\ 1 \end{array} \begin{array}{r} \phantom{0} \\ 0 \end{array}$$
$$\begin{array}{r} 0025 \\ -15 \\ \hline 10 \end{array} \quad \begin{array}{r} 0 \\ 3 \end{array} \begin{array}{r} 1 \\ 2 \end{array} \begin{array}{r} \phantom{0} \\ 1 \end{array} \begin{array}{r} \phantom{0} \\ 0 \end{array}$$
$$\begin{array}{r} 0108 \\ -105 \\ \hline 3 \end{array} \quad \begin{array}{r} 0 \\ 3 \end{array} \begin{array}{r} 1 \\ 2 \end{array} \begin{array}{r} 7 \\ 1 \end{array} \begin{array}{r} \phantom{0} \\ 0 \end{array}$$
$$\begin{array}{r} 0034 \\ -30 \\ \hline 4 \end{array} \quad \begin{array}{r} 0 \\ 3 \end{array} \begin{array}{r} 1 \\ 2 \end{array} \begin{array}{r} 7 \\ 1 \end{array} \begin{array}{r} 2 \\ 0 \end{array}$$

# Divider

$$A/B = Q + R$$

Decimal:

$$2584/15 = 172 \text{ R}4$$

$\begin{array}{r} 0002 \\ - 15 \\ \hline -13 \end{array}$	$\begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$
$\begin{array}{r} 0025 \\ - 15 \\ \hline 10 \end{array}$	$\begin{array}{r} 0 \phantom{0} \\ \hline 3 \end{array} \begin{array}{r} 1 \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$
$\begin{array}{r} 0108 \\ - 105 \\ \hline 3 \end{array}$	$\begin{array}{r} 0 \phantom{0} \phantom{0} \\ \hline 3 \end{array} \begin{array}{r} 1 \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} 7 \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$
$\begin{array}{r} 0034 \\ - 30 \\ \hline 4 \end{array}$	$\begin{array}{r} 0 \phantom{0} \phantom{0} \phantom{0} \\ \hline 3 \end{array} \begin{array}{r} 1 \phantom{0} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} 7 \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} 2 \\ \hline 0 \end{array}$

Binary:

$$1101/10 = 0110 \text{ R}1$$

$\begin{array}{r} 0001 \\ - 0010 \\ \hline 1111 \end{array}$	$\begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$
$\begin{array}{r} 0011 \\ - 0010 \\ \hline 0001 \end{array}$	$\begin{array}{r} 0 \phantom{0} \\ \hline 3 \end{array} \begin{array}{r} 1 \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$
$\begin{array}{r} 0010 \\ - 0010 \\ \hline 0000 \end{array}$	$\begin{array}{r} 0 \phantom{0} \phantom{0} \\ \hline 3 \end{array} \begin{array}{r} 1 \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} 1 \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$
$\begin{array}{r} 0001 \\ - 0010 \\ \hline 1111 \end{array}$	$\begin{array}{r} 0 \phantom{0} \phantom{0} \phantom{0} \\ \hline 3 \end{array} \begin{array}{r} 1 \phantom{0} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} 1 \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} 0 \\ \hline 0 \end{array} \text{ R}1$

# Divider

$$A/B = Q + R/B$$

$$R' = 0$$

for  $i = N-1$  to 0

$$R = \{R' \ll 1, A_i\}$$

$$D = R - B$$

if  $D < 0$ ,  $Q_i = 0$ ;  $R' = R$

else  $Q_i = 1$ ;  $R' = D$

$$R' = R$$

**Binary:**  $1101/10 = 0110$

**R1**

$$\begin{array}{r} 0001 \\ -0010 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} \phantom{0} \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0011 \\ -0010 \\ \hline 0001 \end{array}$$

$$\begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} 1 \\ \hline 2 \end{array} \begin{array}{r} \phantom{0} \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$$


$$\begin{array}{r} 0010 \\ -0010 \\ \hline 0000 \end{array}$$

$$\begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} 1 \\ \hline 2 \end{array} \begin{array}{r} 1 \\ \hline 1 \end{array} \begin{array}{r} \phantom{0} \\ \hline 0 \end{array}$$


$$\begin{array}{r} 0001 \\ -0010 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} 0 \\ \hline 3 \end{array} \begin{array}{r} 1 \\ \hline 2 \end{array} \begin{array}{r} 1 \\ \hline 1 \end{array} \begin{array}{r} 0 \\ \hline 0 \end{array} \text{ R1}$$

# 4x4 Divider

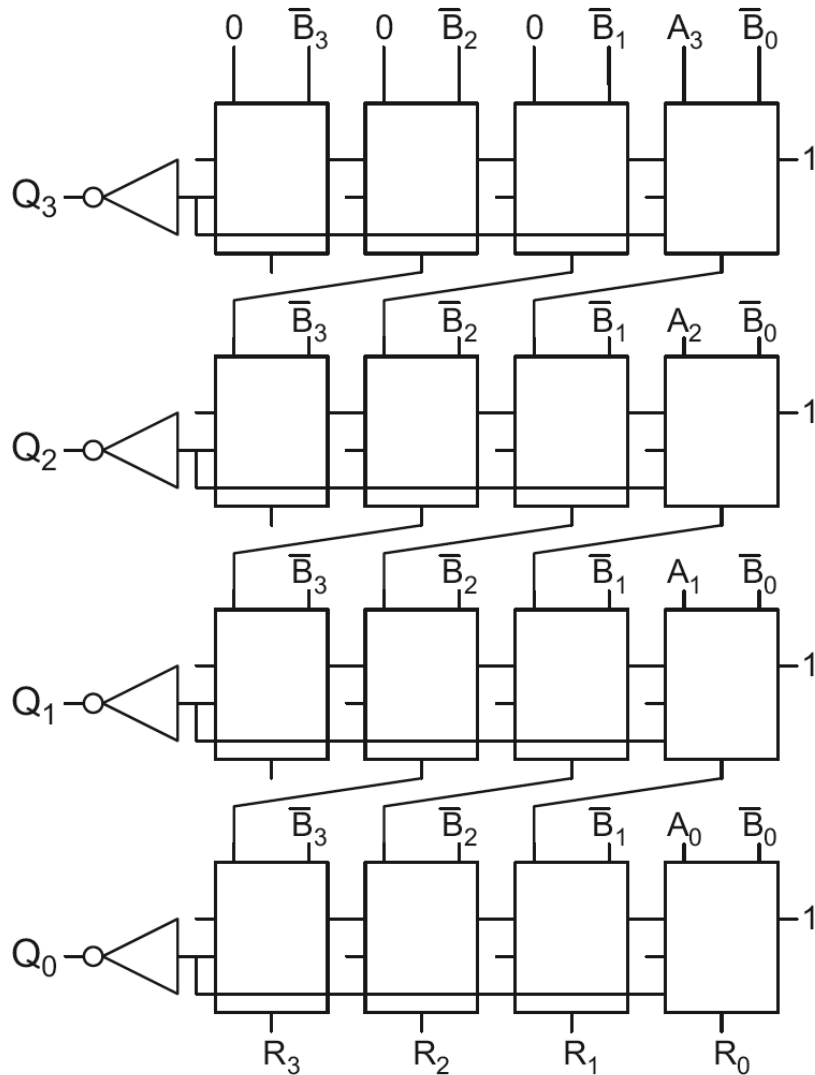

Legend

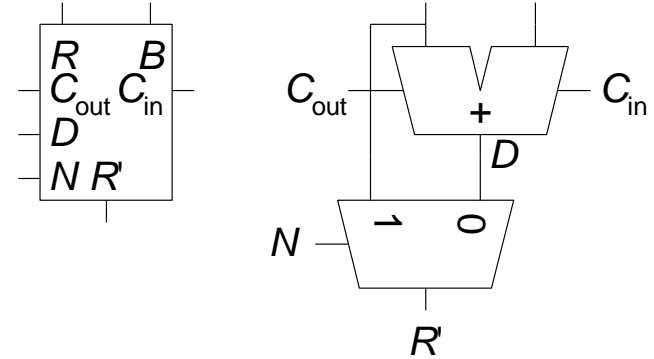

**Division:**  $A/B = Q + R/B$

$R' = 0$

for  $i = N-1$  to  $0$

$R = \{R' \ll 1, A_i\}$

$D = R - B$



if  $D < 0$ ,  $Q_i = 0$ ,  $R' = R$

else  $Q_i = 1$ ,  $R' = D$

$R' = R$

Each row computes one iteration of the division algorithm.


# Sequential division

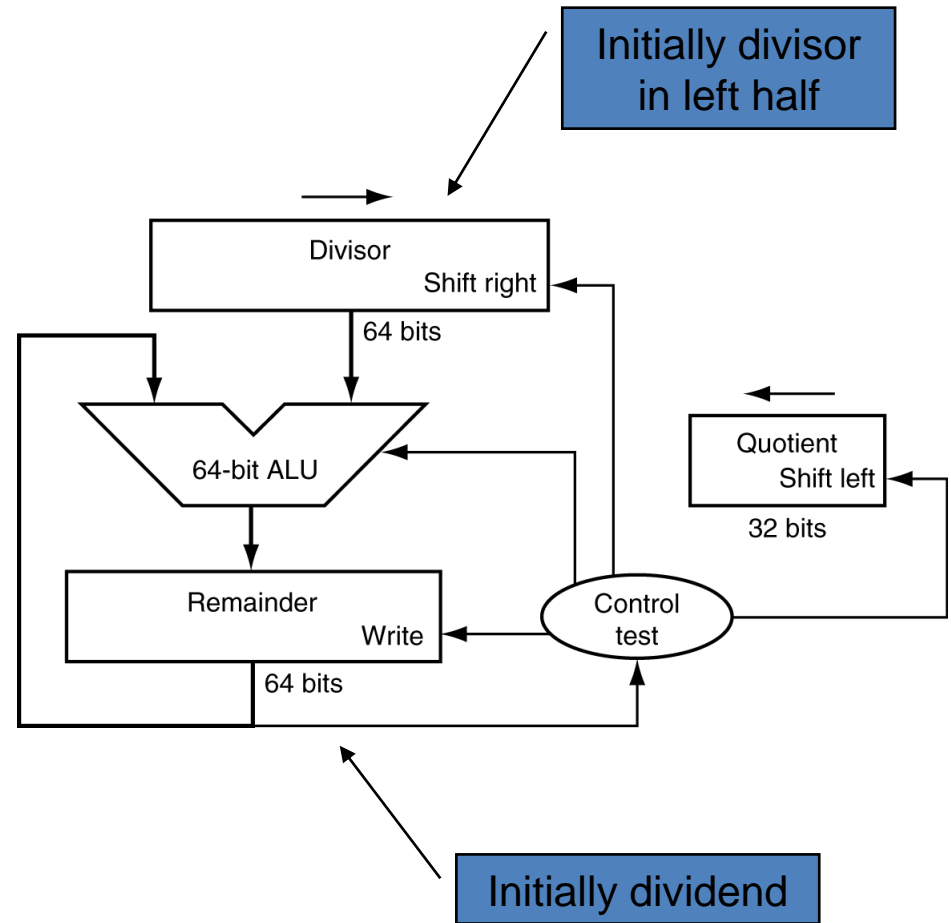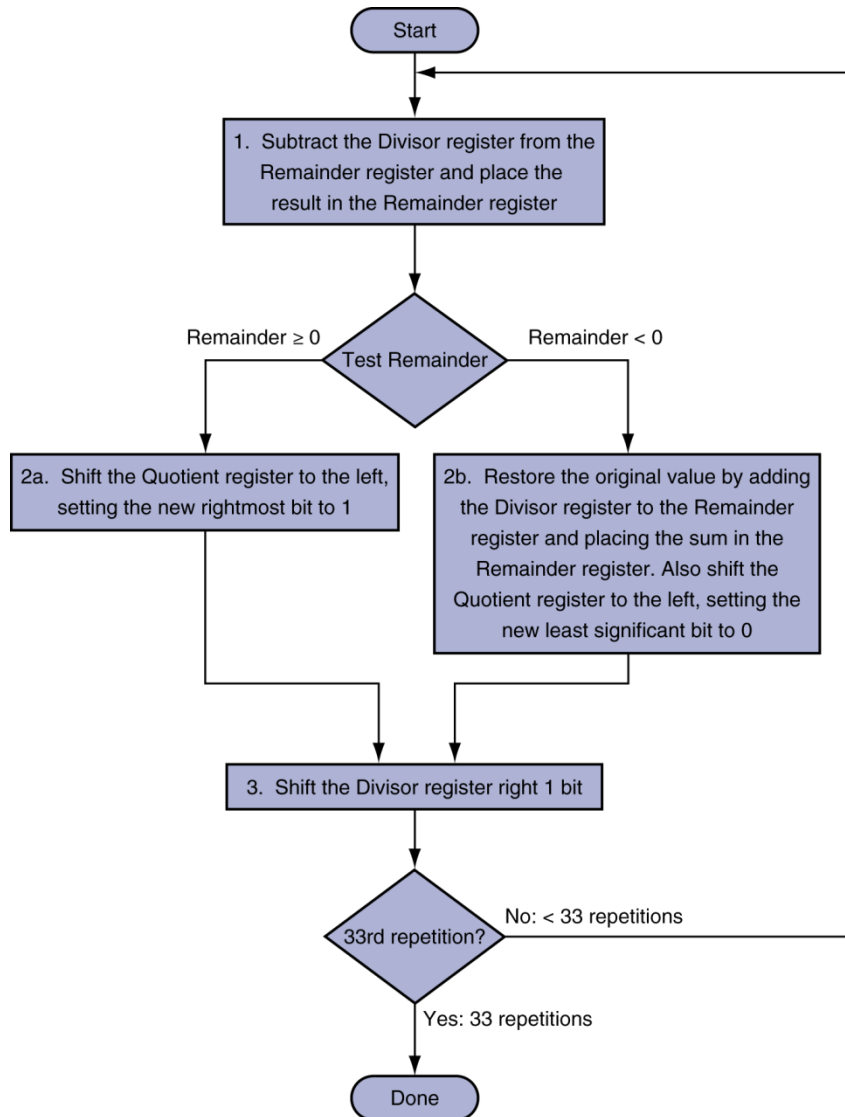


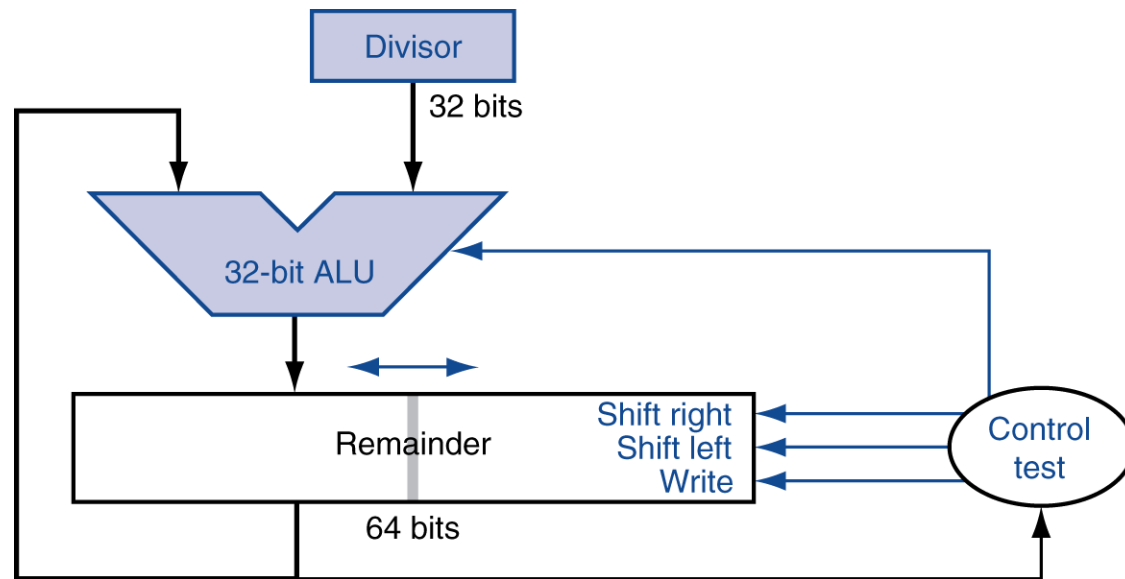
# Optimized divider

- One cycle per partial-remainder subtraction
- Looks a lot like a multiplier!
  - Same hardware can be used for both



# Faster Division

- Can't use parallel hardware as in multiplier
  - Subtraction is conditional on sign of remainder
- Faster dividers generate multiple quotient bits per step
  - Still require multiple steps