

TC2009B: Digital design Addition & Subtraction

Isaac Pérez Andrade

ITESM Guadalajara
School of Engineering & Science
Department of Computer Science
August – December 2021



References

The following material has been adopted and adapted from


Patterson, D. A., Hennessy, J. L., *Computer Organization and design: The hardware/software interface – ARM edition*, Morgan Kaufmann, 2017.

S. L. Harris and D. M. Harris, *Digital design and computer architecture - ARM edition*, Morgan Kaufmann, 2016.

Adder

1-bit adders

Half Adder

 


A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		

S =

C_{out} =

Full Adder

 


C_{in}	A	B	C_{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

S =

C_{out} =

1-bit adders

Half Adder

 


A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

S =

C_{out} =

Full Adder

 


C _{in}	A	B	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

S =

C_{out} =

1-bit adders

Half Adder

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

Full Adder

 


C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$


Multibit adders

 - Types of carry propagate adders (CPAs):
 - Ripple-carry (slow)
 - Carry-lookahead (fast)
 - Prefix (faster)
- Carry-lookahead and prefix adders faster for large adders but require more hardware



Ripple-Carry adder

 - Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



- $t_{ripple} = Nt_{FA}$
 t_{FA} is the delay of a 1-bit full adder

Carry-lookahead adder

Compute C_{out} for k -bit blocks using *generate* and *propagate* signals

- **Some definitions:**

- Column i produces a carry out by either *generating* a carry out or *propagating* a carry in to the carry out
- Generate (G_i) and propagate (P_i) signals for each column:
 - **Generate:** Column i will generate a carry out if A_i **and** B_i are both 1.

$$G_i = A_i B_i$$

- **Propagate:** Column i will propagate a carry in into the carry out if A_i **or** B_i is 1.

$$P_i = A_i + B_i$$

- **Carry out:** The carry out of column i (C_i) is:

$$C_i = A_i B_i + (A_i + B_i) C_{i-1} = G_i + P_i C_{i-1}$$

Carry-lookahead adder

- Now use column **propagate** and **generate** signals to compute **block propagate** and **block generate** signals for k-bit blocks, *i.e.*:
 - Compute if a k-bit group will propagate a carry in (to the block) to the carry out (of the block)
 - Compute if a k-bit group will generate a carry out (of the block)

Carry-lookahead adder

- **Example:** Block propagate and generate signals for 4-bit blocks ($P_{3:0}$ and $G_{3:0}$):

$$P_{3:0} = P_3 P_2 P_1 P_0$$

$$G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$$


- Generally,

$$P_{i:j} = P_i P_{i-1} P_{i-2} \dots P_j$$

$$G_{i:j} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} (G_{i-3} + P_{i-3} (\dots G_{j+1} + P_{j+1} G_j)))$$

$$C_i = G_{i:j} + P_{i:j} C_{i-1}$$

32-bit Carry-lookahead with 4 blocks

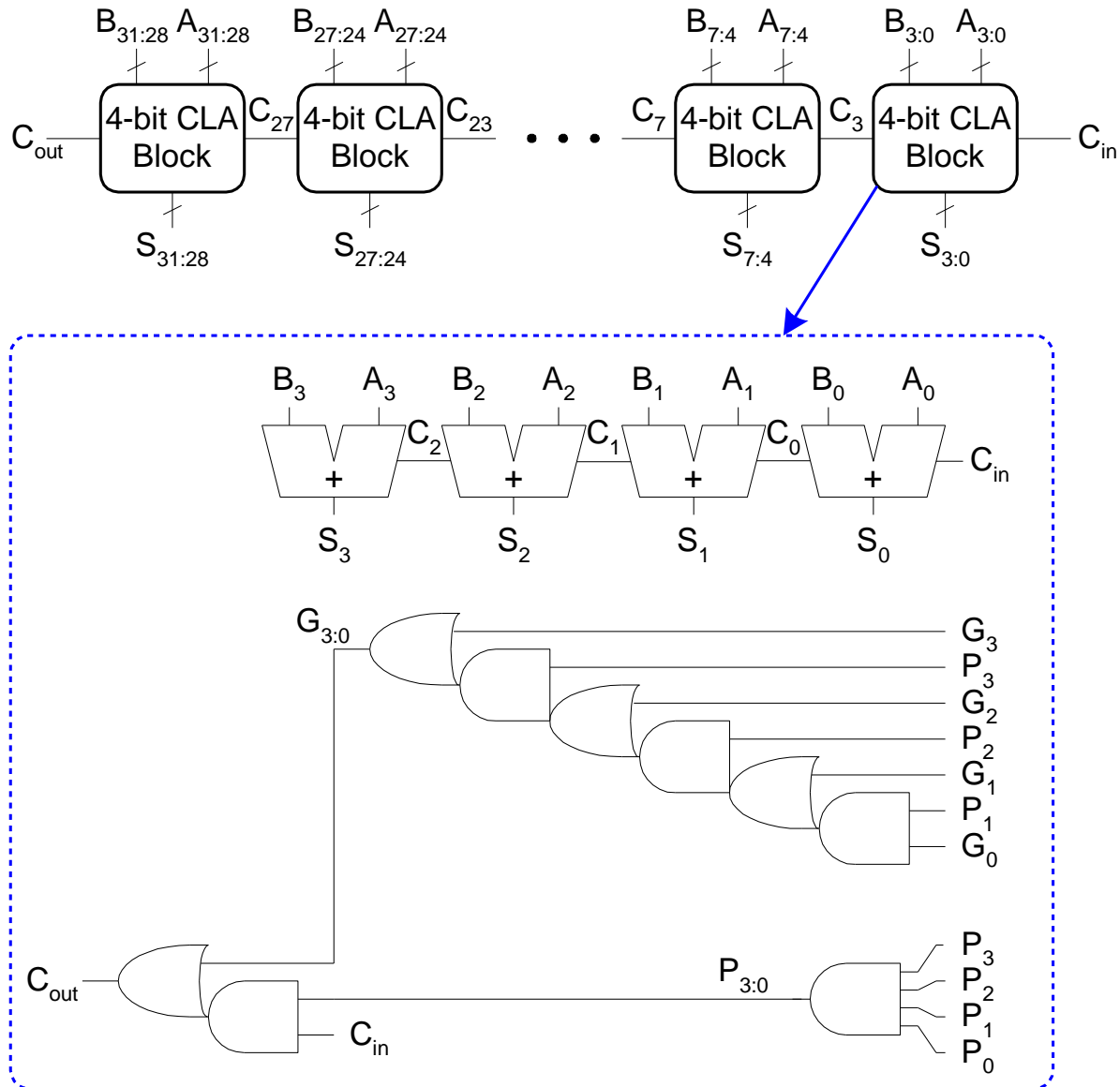

Carry-lookahead addition

- **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate logic (meanwhile computing sums)
- **Step 4:** Compute sum for most significant k -bit block

Carry-lookahead adder delay

- For N -bit CLA with k -bit blocks:

$$t_{CLA} = t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA}$$

where:

- t_{pg} : delay to generate all P_i and G_i
 - t_{pg_block} : delay to generate all $P_{i:j}$ and $G_{i:j}$
 - t_{AND_OR} : delay from C_{in} to C_{out} of final AND/OR gate in k -bit CLA block
- An N -bit carry-lookahead adder is generally much faster than a ripple-carry adder for $N > 16$

Prefix adder

- Computes carry in (C_{i-1}) for each column, then computes sum:

$$S_i = (A_i \oplus B_i) \oplus C_i$$

- It computes C_{i-1} by:
 - Computing G and P for 1-, 2-, 4-, 8-bit blocks, etc. until all G_i (carry in) known
- $\log_2 N$ stages

Prefix adder

- Carry is either *generated* in a column or *propagated* from a previous column.
- Column -1 holds C_{in} , so

$$G_{-1} = C_{in}$$

$$P_{-1} = 0$$

- Carry in into column i = carry out of column $i-1$:

$$C_{i-1} = G_{i-1:-1}$$

- $G_{i-1:-1}$: generate signal spanning columns $i-1$ to -1
- Sum equation:

$$S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$$

- **Goal:** Quickly compute $G_{0:-1}, G_{1:-1}, G_{2:-1}, G_{3:-1}, G_{4:-1}, G_{5:-1}, \dots$
(called *prefixes*) $(C_0, C_1, C_2, C_3, C_4, C_5,)$

Prefix adder


- Generate and propagate signals for a block spanning bits $i:j$

$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$




$$P_{i:j} = P_{i:k} P_{k-1:j}$$

- In words:
 - **Generate:** block $i:j$ will generate a carry if:
 - upper part ($i:k$) generates a carry or
 - upper part ($i:k$) propagates a carry generated in lower part ($k-1:j$)
 - **Propagate:** block $i:j$ will propagate a carry if *both* the upper and lower parts propagate the carry

16-bit prefix adder

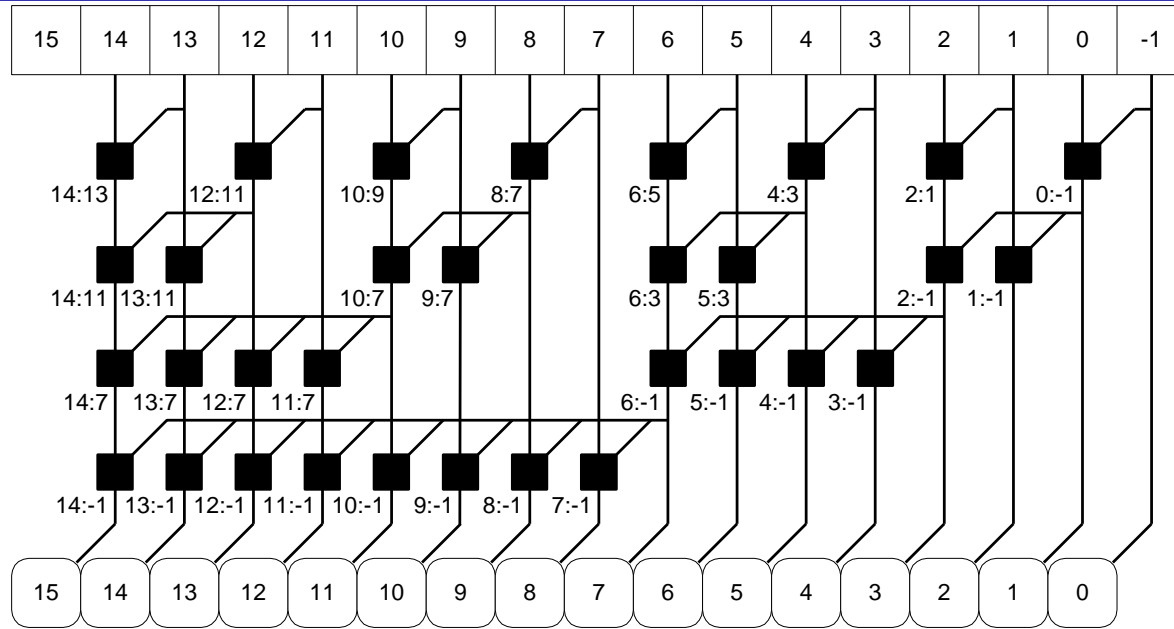

Legend

   

Prefix adder delay

$$t_{PA} = t_{pg} + \log_2 N(t_{pg_prefix}) + t_{XOR}$$

- t_{pg} : delay to produce P_i, G_i (AND or OR gate)
- t_{pg_prefix} : delay of black prefix cell (AND-OR gate)

Adder delay comparison

Compare delay of 32-bit adder structures: ripple-carry, carry-lookahead, and prefix adders

- Carry-lookahead has 4-bit blocks
- 2-input gate delay = 100 ps;
- full adder delay = 300 ps

$$\begin{aligned}t_{\text{ripple}} &= Nt_{FA} = 32(300 \text{ ps}) \\ &= \mathbf{9.6 \text{ ns}}\end{aligned}$$


$$\begin{aligned}t_{CLA} &= t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA} \\ &= [100 + 600 + (7)200 + 4(300)] \text{ ps} \\ &= \mathbf{3.3 \text{ ns}}\end{aligned}$$

$$\begin{aligned}t_{PA} &= t_{pg} + \log_2 N(t_{pg_prefix}) + t_{XOR} \\ &= [100 + \log_2 32(200) + 100] \text{ ps} \\ &= \mathbf{1.2 \text{ ns}}\end{aligned}$$


Misc arithmetic circuits

Subtractor

Symbol

 


Implementation

 


Comparator

Symbol

 

Implementation

 

Adder/subtractor circuit

- How can we implement an adder/subtractor circuit reutilizing adder's HW?